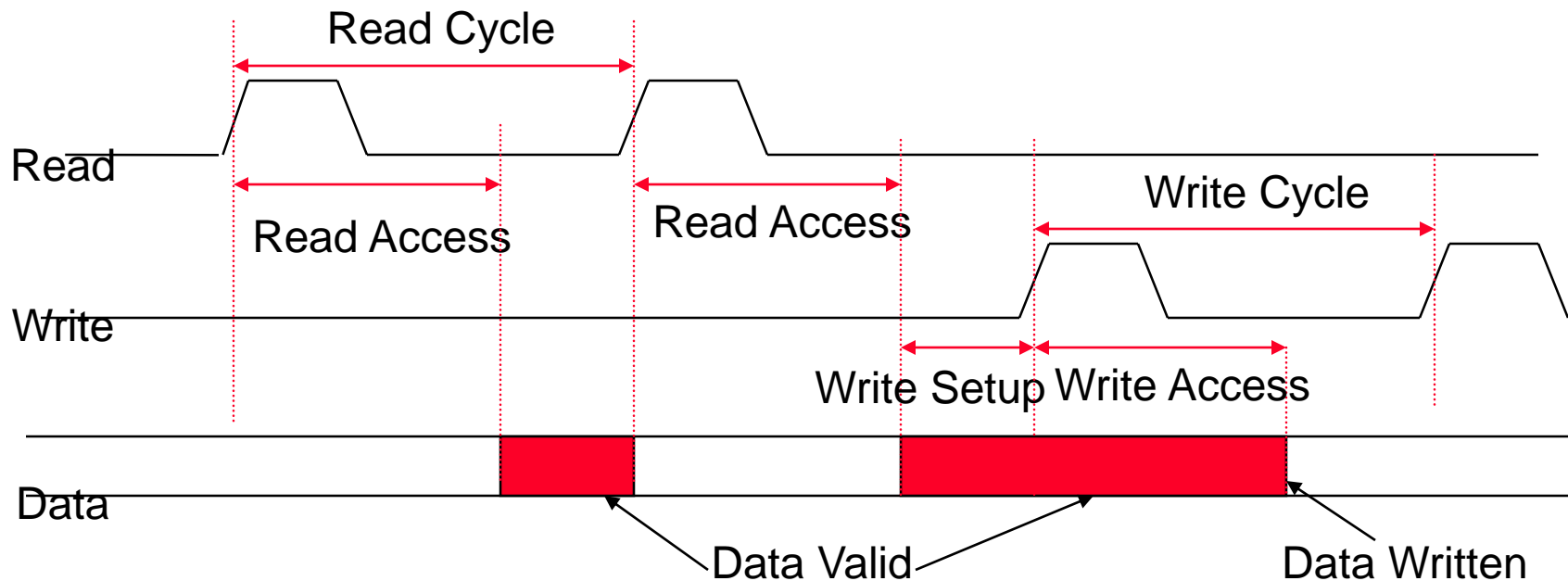

VLSI Digital Circuits

Memory Cell Designs

Link: <https://uweb.engr.arizona.edu/~ece507/lecture16.ppt>


Memory Definitions

- ❑ Size – Kbytes, Mbytes, Gbytes, Tbytes
- ❑ Speed
 - ❑ Read Access – delay between read request and the data available
 - ❑ Write Access – delay between write request and the writing of the data into the memory
 - ❑ (Read or Write) Cycle - minimum time required between successive reads or writes



A Typical Memory Hierarchy

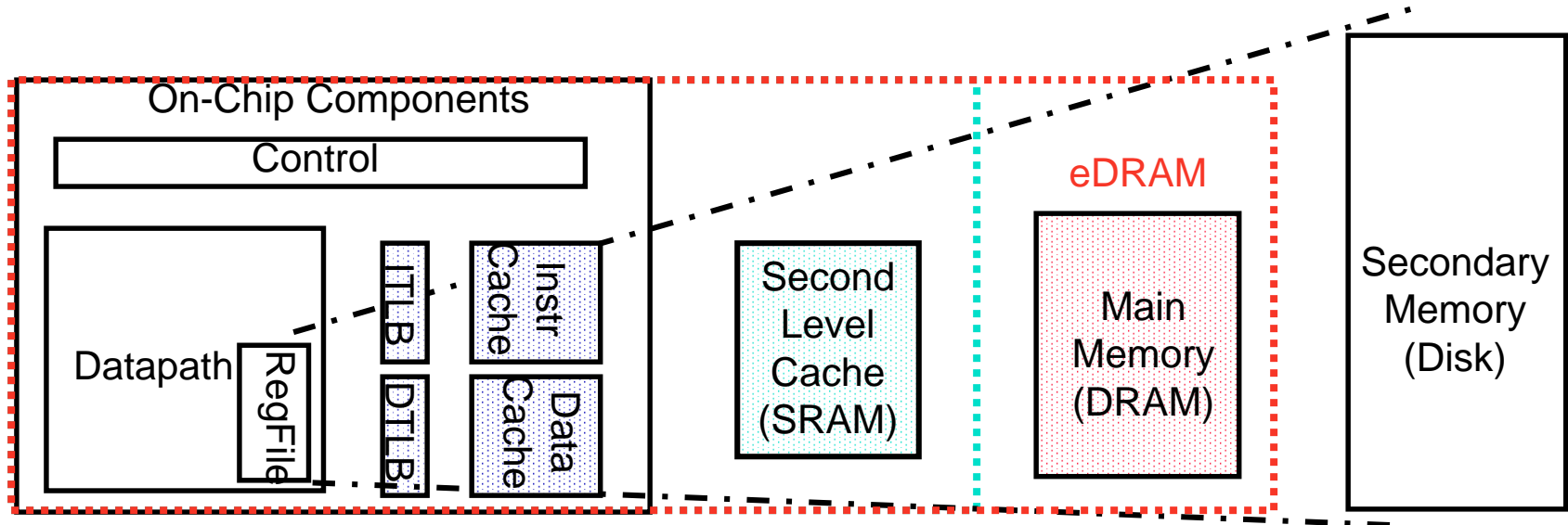- ❑ By taking advantage of the principle of locality, we can
 - ❑ present the user with as much memory as is available in the cheapest technology
 - ❑ at the speed offered by the fastest technology.



Speed (ns):	.1's	1's	10's	100's	1,000's
Size (bytes):	100's	K's	10K's	M's	T's
Cost:	highest				lowest

More Memory Definitions

- ❑ Function – functionality, nature of the storage mechanism
 - ❑ static and dynamic; volatile and nonvolatile (NV); read only (ROM)
- ❑ Access pattern – random, serial, content addressable

Read Write Memories (RWM)		NVRWM	ROM
Random Access	Non-Random Access	EPROM	Mask-prog. ROM
SRAM (cache, register file)	FIFO, LIFO	EEPROM	
DRAM (main memory)	Shift Register	FLASH	Electrically-prog. PROM
CAM			


- ❑ Input-output architecture – number of data input and output ports (multiported memories)
- ❑ Application – embedded, secondary, tertiary

Random Access Read Write Memories (WRMs)


- ❑ SRAM – Static Random Access Memory
 - ❑ data is stored as long as supply is applied
 - ❑ large cells (6 fets/cell) – so fewer bits/chip
 - ❑ fast – so used where speed is important (e.g., caches)
 - ❑ differential outputs (output BL and !BL)
 - ❑ use sense amps for performance
 - ❑ compatible with CMOS technology

- ❑ DRAM - Dynamic Random Access Memory
 - ❑ periodic refresh required (every 1 to 4 ms) to compensate for the charge loss caused by leakage
 - ❑ small cells (1 to 3 fets/cell) – so more bits/chip
 - ❑ slower – so used for main memories
 - ❑ single ended output (output BL only)
 - ❑ need sense amps for correct operation
 - ❑ not typically compatible with CMOS technology


Evolution in DRAM Chip Capacity

 

1D Memory Architecture

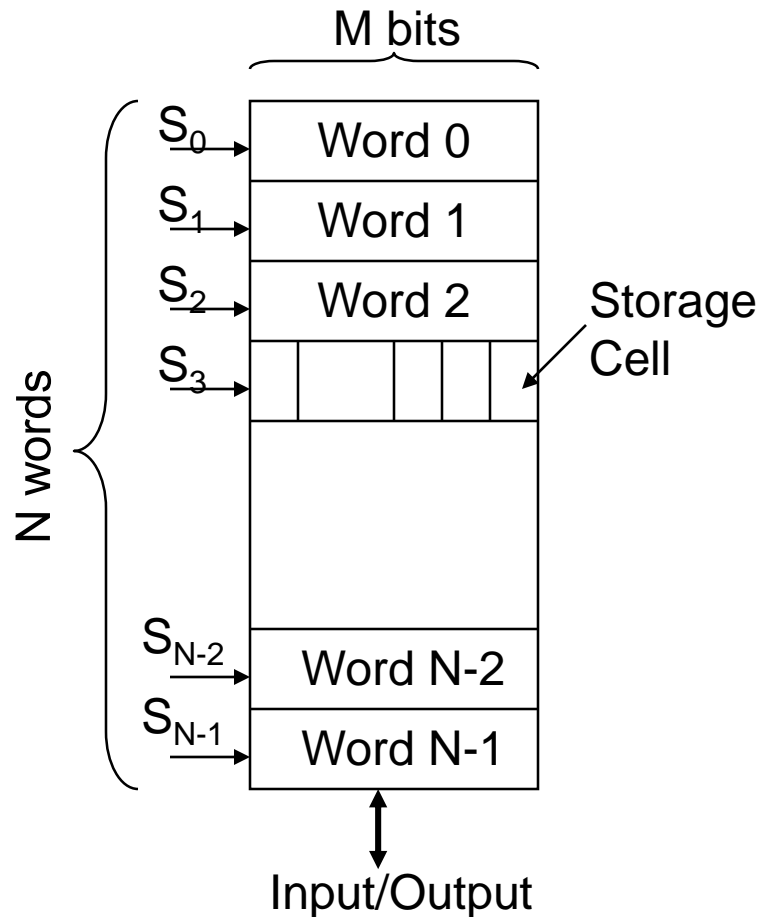


N words \rightarrow N select signals

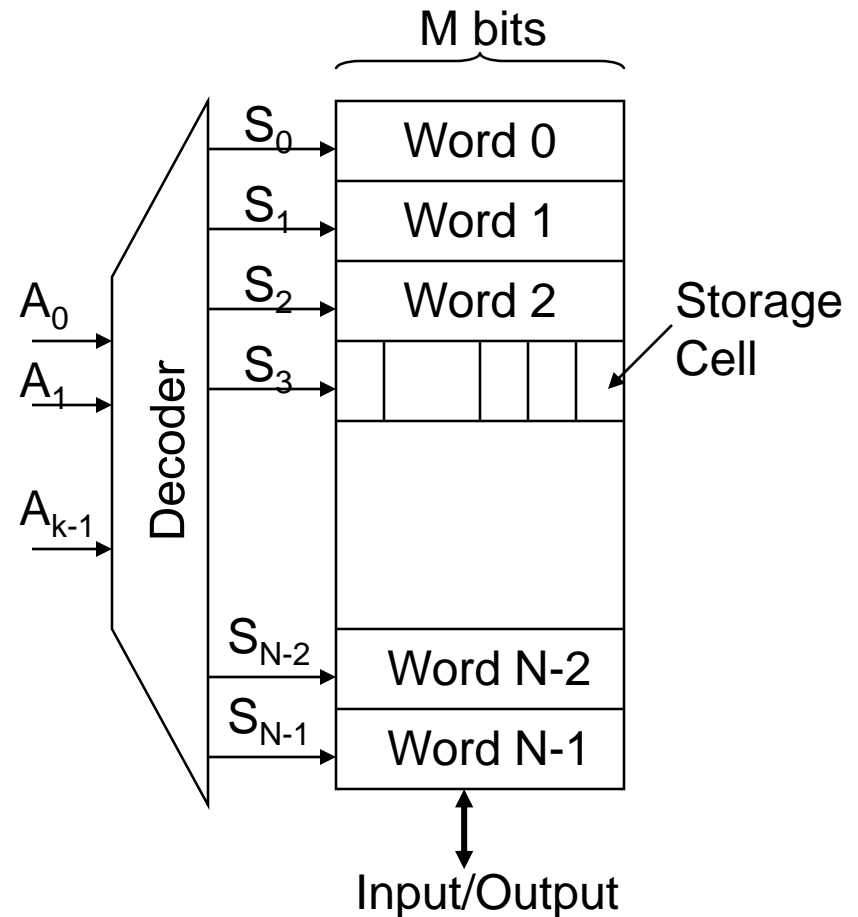


Decoder reduces # of inputs
 $K = \log_2 N$

2D Memory Architecture

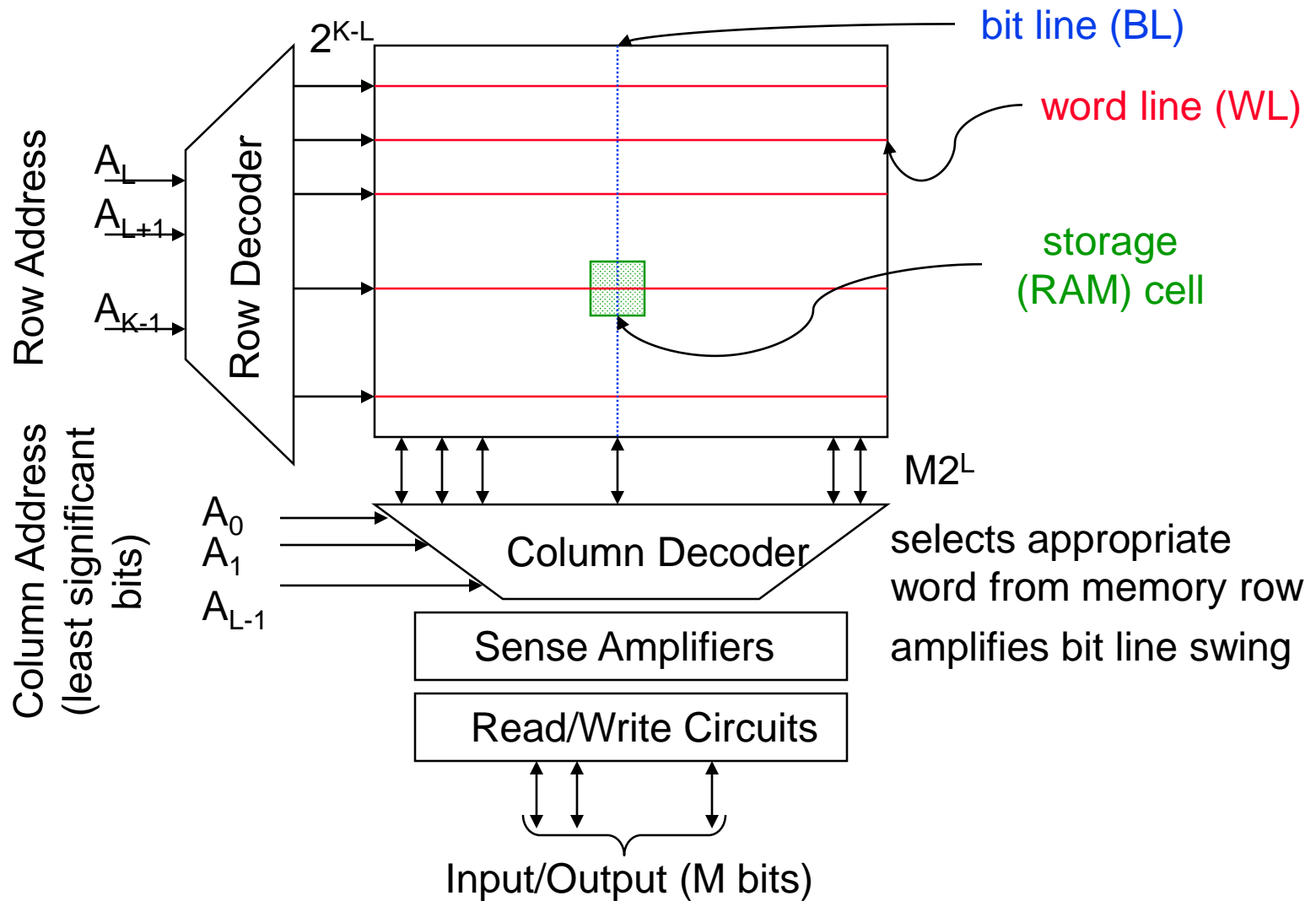


3D (or Banked) Memory Architecture

 


Advantages:

1. Shorter word and bit lines so faster access
2. Block addr activates only 1 block saving power


2D 4x4 SRAM Memory Bank

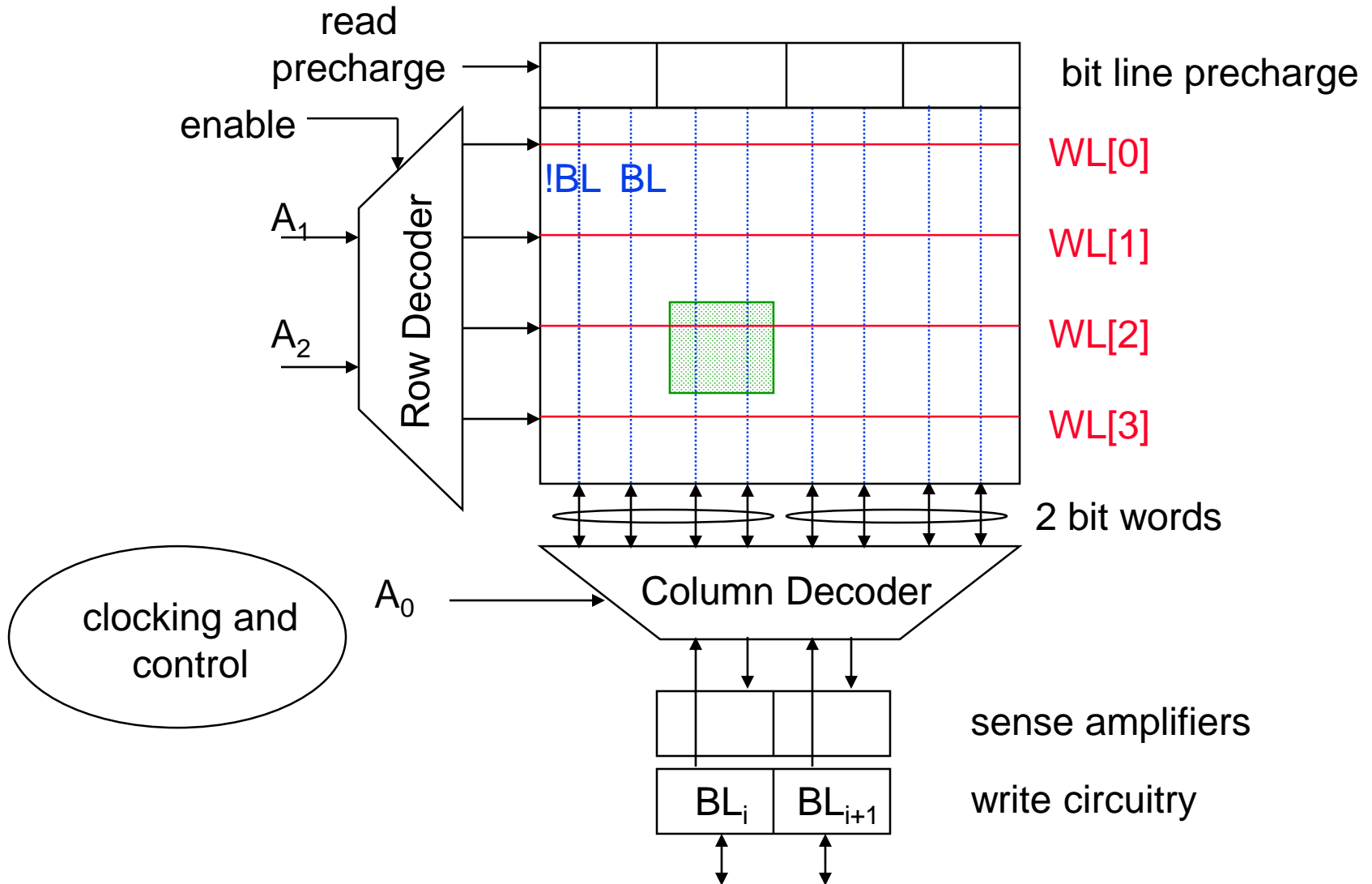


Quartering Gives Shorter WLs and BLs

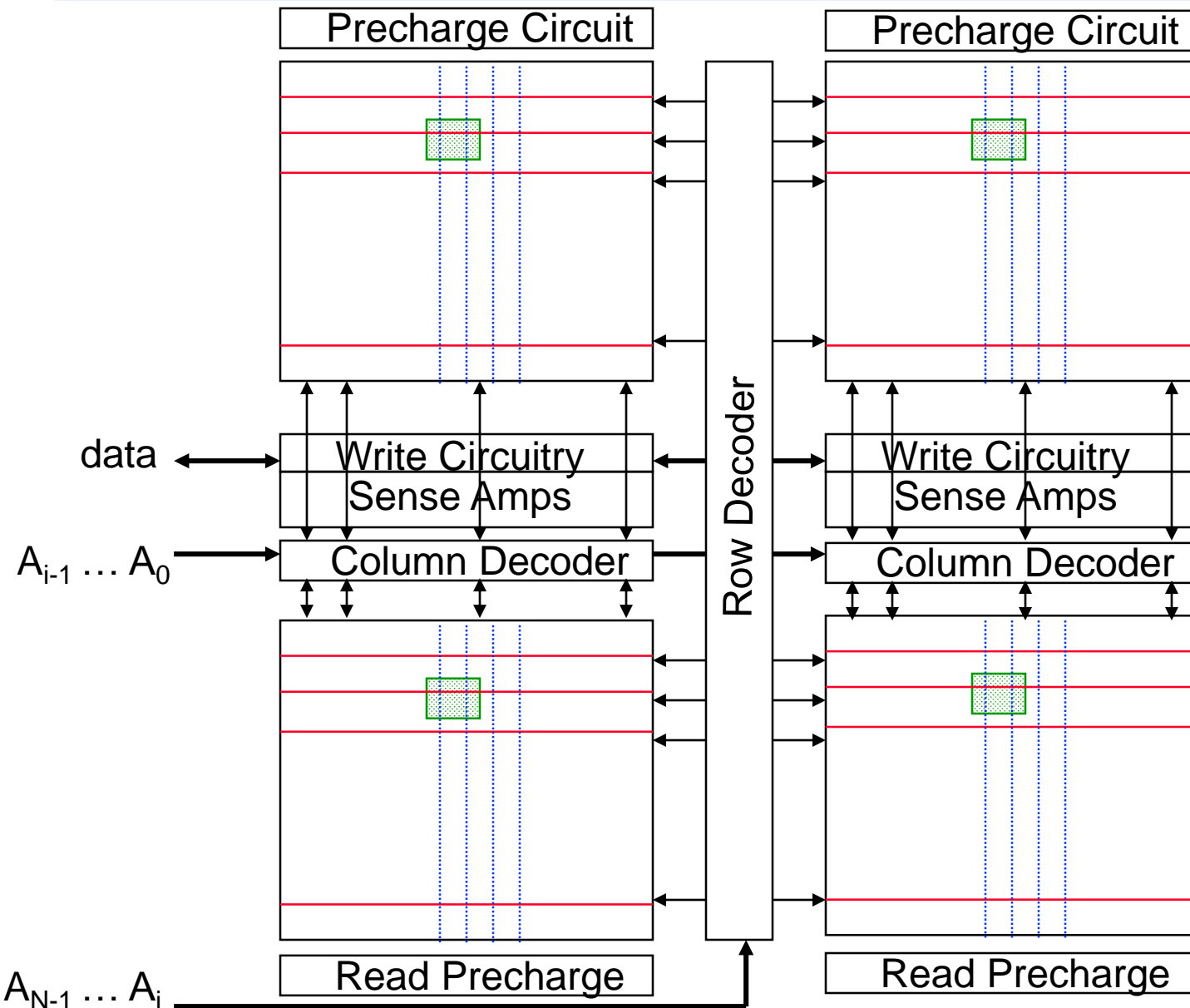

6-Transistor SRAM Storage Cell

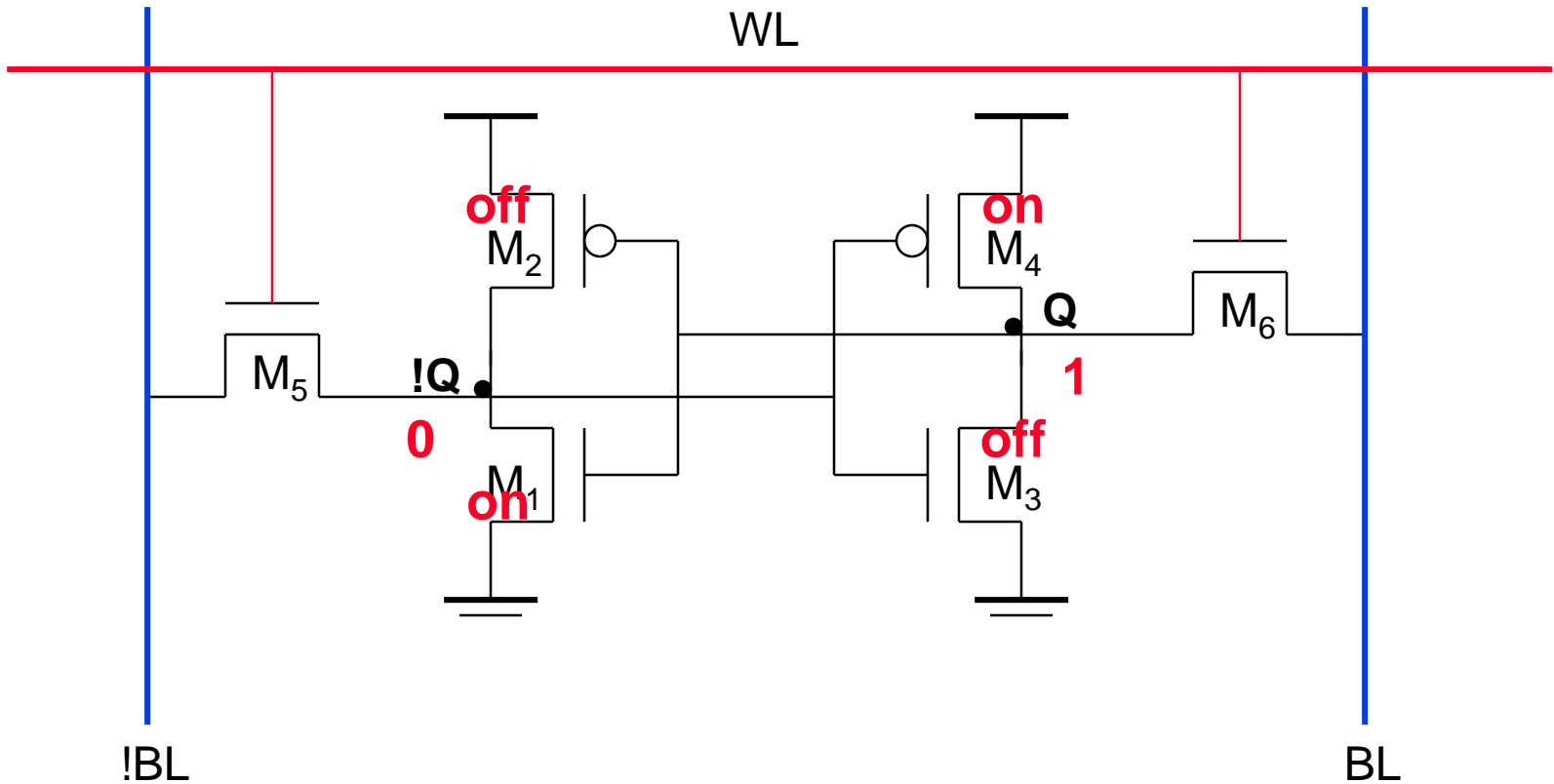

SRAM Cell Analysis (Read)

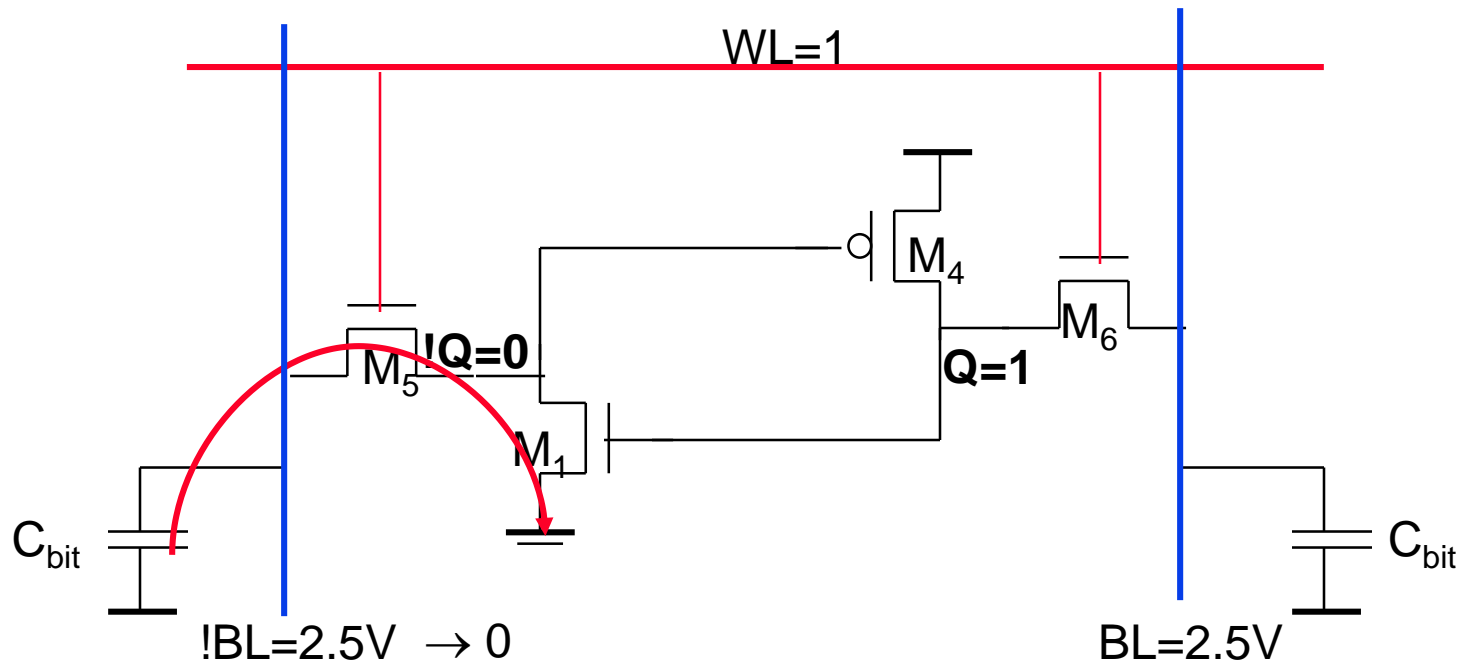


- ❑ **Read-disturb (read-upset):** must limit the voltage rise on !Q to prevent read-upsets from occurring while simultaneously maintaining acceptable circuit speed and area
 - ❑ M_1 must be stronger than M_5 when storing a 1 (as shown)
 - ❑ M_3 must be stronger than M_6 when storing a 0

Read Voltage Ratios

$$\Delta V_{IQ} = [V_{DSATn} + CR(V_{DD} - V_{Tn}) - \sqrt{(V_{DSATn}^2(1+CR) + CR^2(V_{DD} - V_{Tn})^2)}]/CR$$


where CR is the Cell Ratio = $(W_1/L_1)/(W_5/L_5) \geq 1.2$

$$V_{DD} = 2.5V$$
$$V_{Tn} = 0.4V$$

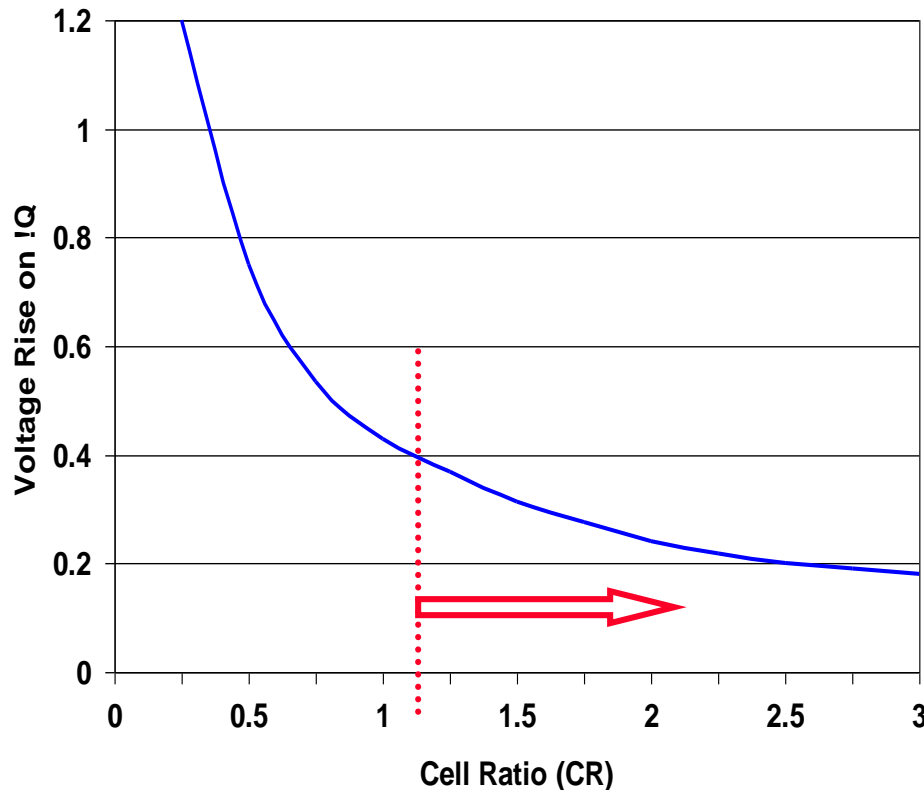

- Keep cell size minimal while maintaining read stability
 - Make M_1 minimum size and increase the L of M_5 (to make it weaker)
 - increases load on WL
 - Make M_5 minimum size and increase the W of M_1 (to make it stronger)
- Similar constraints on $(W_3/L_3)/(W_6/L_6)$ when storing a 0

SRAM Cell Analysis (Write)

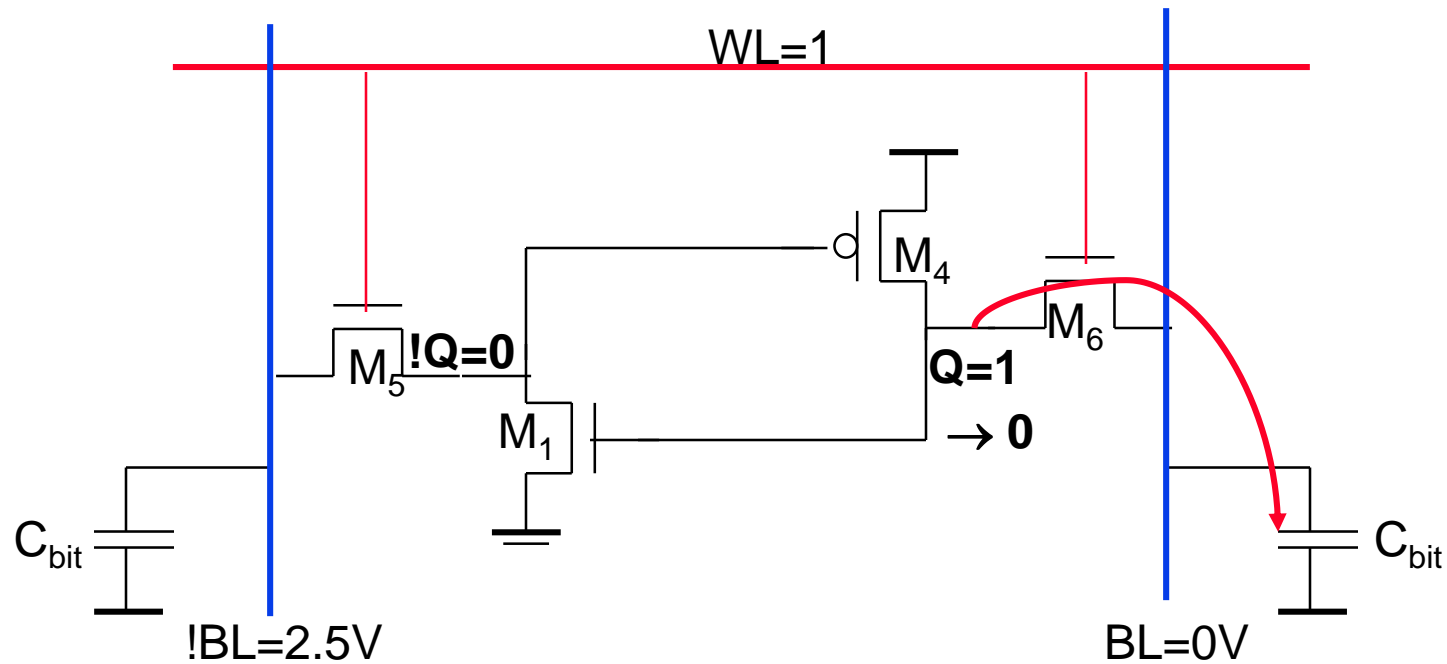

- ❑ The !Q side of the cell cannot be pulled high enough to ensure writing of 0 (because M₁ is on and sized to protect against read upset). So, the new value of the cell has to be **written** through M₆.
 - ❑ M₆ must be able to overpower M₄ when storing a 1 and writing a 0
 - ❑ M₅ must be able to overpower M₂ when storing a 0 and writing a 1

Write Voltage Ratios


$$V_Q = (V_{DD} - V_{Tn}) - \sqrt{((V_{DD} - V_{Tn})^2 - 2(\mu_p/\mu_n)(PR)((V_{DD} - |V_{Tp}|)V_{DSATp} - V_{DSATp}^2/2))}$$

$$V_{DD} = 2.5V$$

$$|V_{Tp}| = 0.4V$$

$$\mu_p/\mu_n = 0.5$$

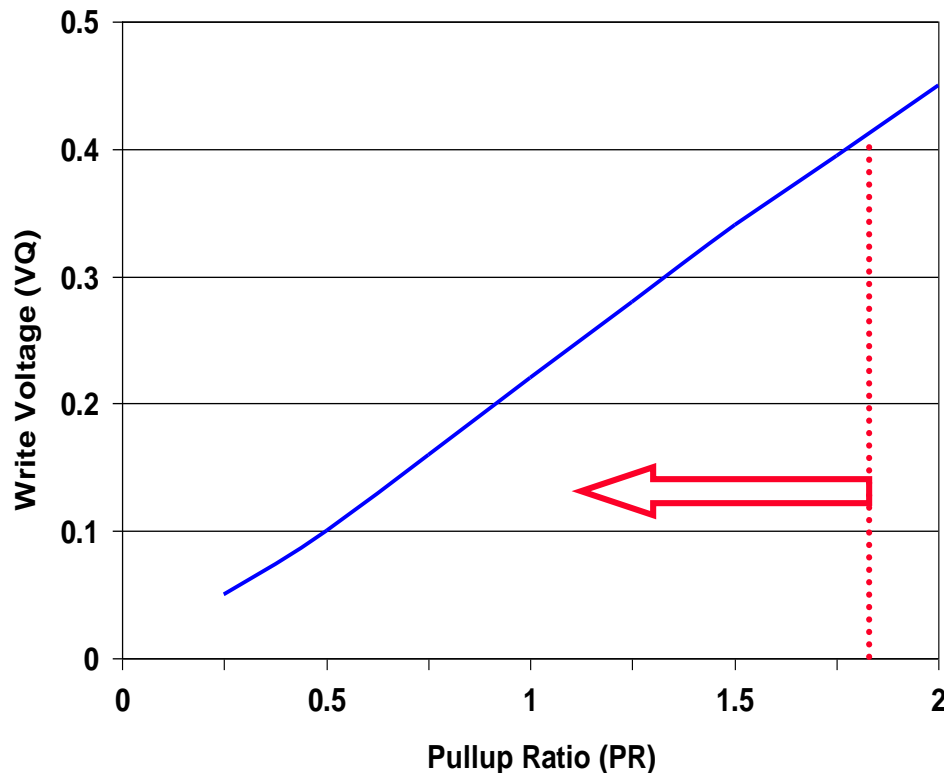where PR is the Pull-up Ratio = $(W_4/L_4)/(W_6/L_6) \leq 1.8$




- ❑ Keep cell size minimal while allowing writes
 - ❑ Make M_4 and M_6 minimum size
- ❑ Be sure to consider worst case process corners (strong PMOS, weak NMOS, high V_{DD})

Cell Sizing and Performance

- ❑ Keeping cell size minimal is critical for large SRAMs
 - ❑ Minimum sized pull down fets (M_1 and M_3)
 - Requires longer than minimum channel length, L , pass transistors (M_5 and M_6) to ensure proper CR
 - But up-sizing L of the pass transistors increases capacitive load on the word lines *and* limits the current discharged on the bit lines both of which can adversely affect the speed of the read cycle
 - ❑ Minimum width and length pass transistors
 - Boost the width of the pull downs (M_1 and M_3)
 - Reduces the loading on the word lines and increases the storage capacitance in the cell – both are good! – but cell size may be slightly larger


- ❑ Performance is determined by the read operation
 - ❑ To accelerate the read time, SRAMs use sense amplifiers (so that the bit line doesn't have to make a full swing)

6-T SRAM Layout

 


- ❑ Simple and reliable, but big
 - ❑ signal routing and connections to two bit lines, a word line, and both supply rails
- ❑ Area is dominated by the wiring and contacts (11.5 of them)
- ❑ Other alternatives to the 6-T cell include the resistive load 4-T cell and the TFT cell neither of which are available in a standard CMOS logic process

Multiple Read/Write Port Storage Cell


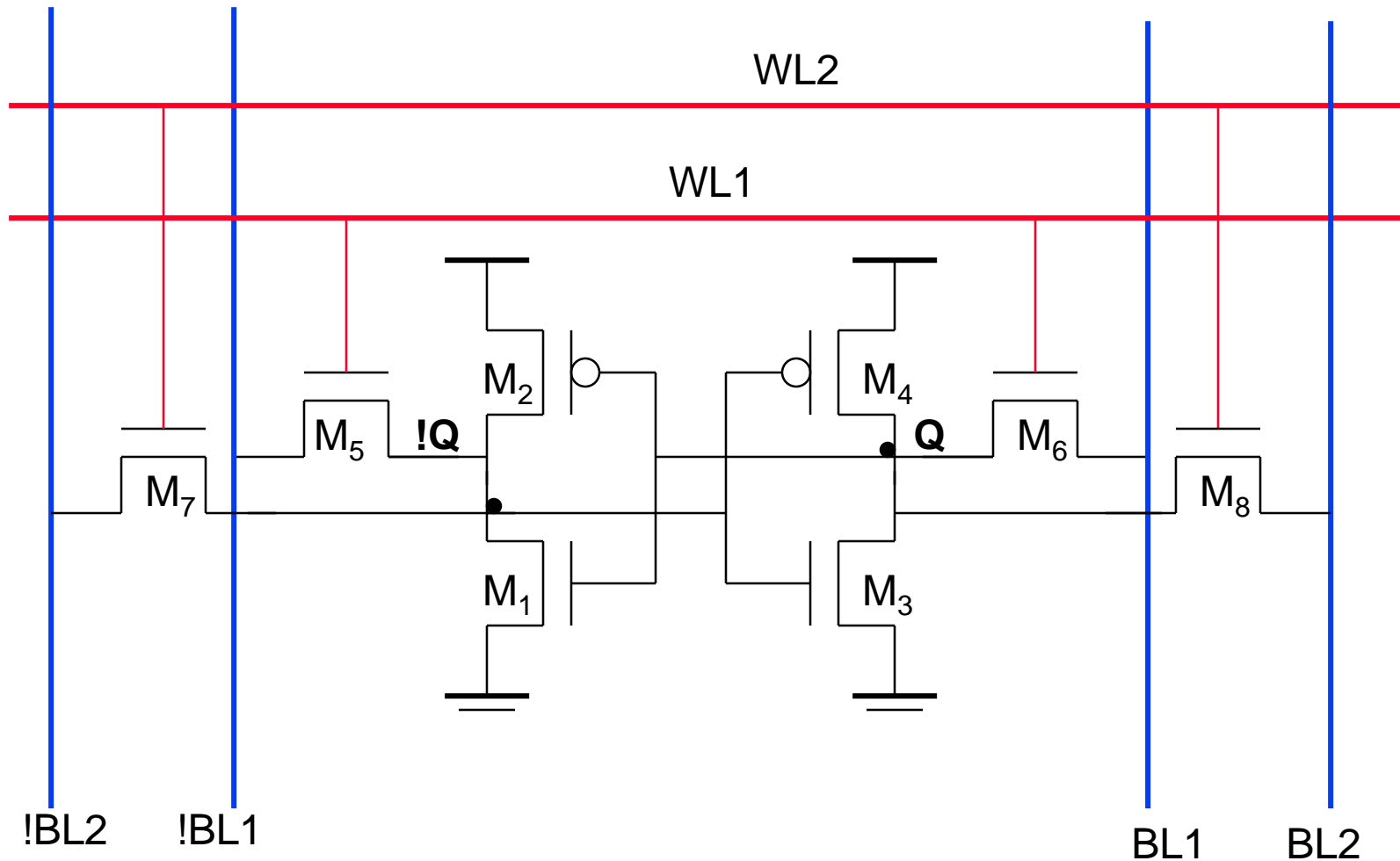


- ❑ To avoid read upset, the widths of M_1 and M_3 will have to be sized up by a factor equal to the number of simultaneously open read ports

2D 4x4 DRAM Memory

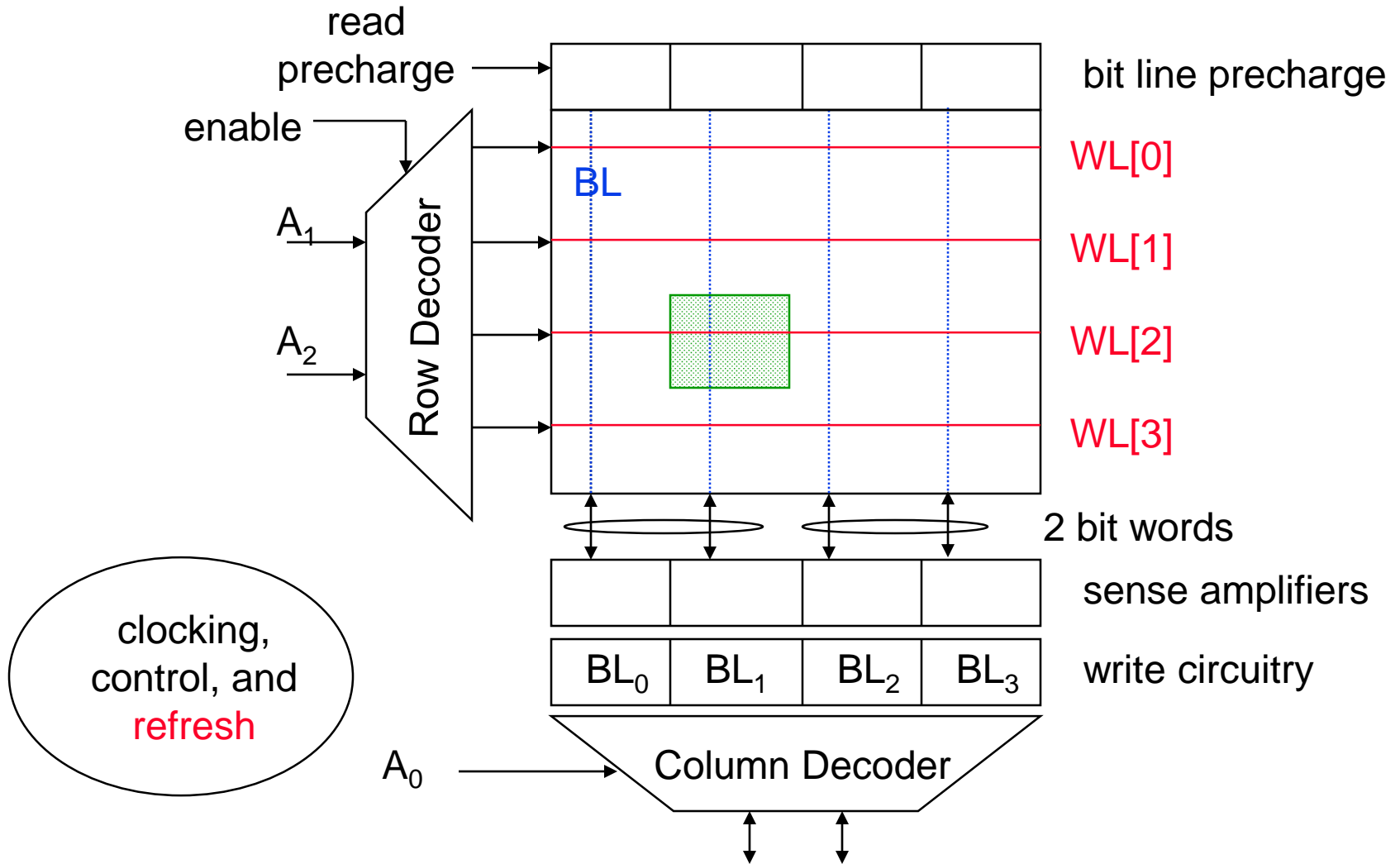


3-Transistor DRAM Cell

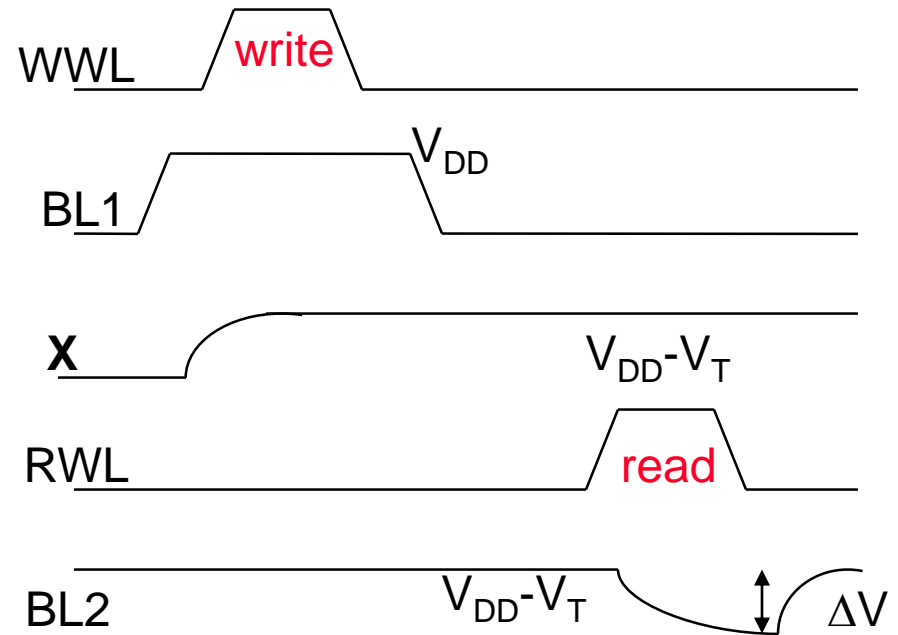 



- Write: C_s is charged (or discharged) by asserting WWL and BL1
 - Value stored at node X when writing a 1 is $V_{WWL} - V_{Tn}$
- Read: C_s is “sensed” by asserting RWL and observing BL2
 - Read is non-destructive and inverting

3-T DRAM Layout

 

- ❑ Total cell area is $576 \lambda^2$ (compared to $1,092 \lambda^2$ for the 6-T SRAM cell)
- ❑ No special processing steps are needed (so compatible with logic CMOS process)
- ❑ Can use bootstrapping (raise V_{WWL} to a value higher than V_{DD}) to eliminate threshold drop when storing a “1”

1-Transistor DRAM Cell

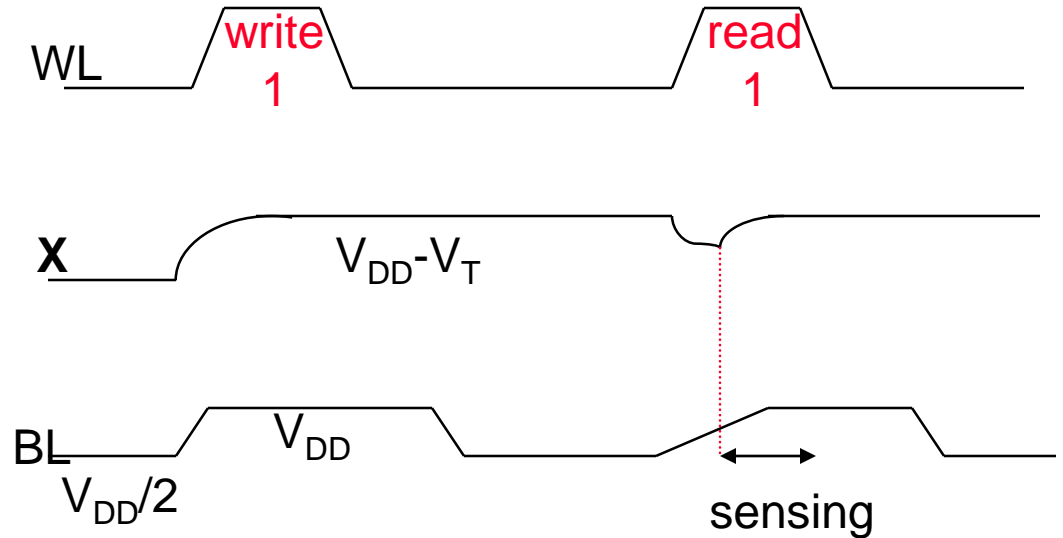 

- ❑ **Write:** C_s is charged (or discharged) by asserting WL and BL
- ❑ **Read:** Charge redistribution occurs between C_{BL} and C_s
 - ❑ Read is destructive, so must refresh after read

1-T DRAM Cell Observations

- ❑ Cell is single ended (complicates the design of the sense amp)
- ❑ Cell **requires** a sense amp for each bit line due to charge redistribution based read
 - ❑ BL's precharged to $V_{DD}/2$ (not V_{DD} as with SRAM design)
 - ❑ all previous designs used SAs for speed, not functionality
- ❑ Cell read is destructive; refresh must follow to restore data
- ❑ Cell requires an extra capacitor (C_S) that must be explicitly included in the design
 - ❑ not compatible with logic CMOS process
- ❑ A threshold voltage is lost when writing a 1 (can be circumvented by bootstrapping the word lines to a higher value than V_{DD})

Peripheral Memory Circuitry

- ❑ Row and column decoders
- ❑ Read bit line precharge logic
- ❑ Sense amplifiers
- ❑ Read/write circuitry
- ❑ Timing and control
- ❑ Speed
- ❑ Power consumption
- ❑ Area – pitch matching

Row Decoders

- ❑ Collection of 2^M complex logic gates organized in a regular, dense fashion

- ❑ (N)AND decoder for 8 address bits

$$WL(0) = !A_7 \& !A_6 \& !A_5 \& !A_4 \& !A_3 \& !A_2 \& !A_1 \& !A_0$$

...

$$WL(255) = A_7 \& A_6 \& A_5 \& A_4 \& A_3 \& A_2 \& A_1 \& A_0$$

- ❑ NOR decoder for 8 address bits

$$WL(0) = !(A_7 \mid A_6 \mid A_5 \mid A_4 \mid A_3 \mid A_2 \mid A_1 \mid A_0)$$

...

$$WL(255) = !(!A_7 \mid !A_6 \mid !A_5 \mid !A_4 \mid !A_3 \mid !A_2 \mid !A_1 \mid !A_0)$$


- ❑ Goals: **Pitch matched**, fast, low power

Implementing a Wide NOR Function


- ❑ Single stage 8x256 bit decoder (as in Lecture 22)
 - ❑ One 8 input NOR gate per row x 256 rows = $256 \times (8+8) = 4,096$
 - ❑ Pitch match and speed/power issues
- ❑ Decompose logic into multiple levels
$$!WL(0) = !(!(A_7 | A_6) \& !(A_5 | A_4) \& !(A_3 | A_2) \& !(A_1 | A_0))$$
 - ❑ First level is the **predecoder** (for each pair of address bits, form $A_i | A_{i-1}$, $A_i | !A_{i-1}$, $!A_i | A_{i-1}$, and $!A_i | !A_{i-1}$)
 - ❑ Second level is the word line driver
- ❑ Predecoders reduce the number of transistors required
 - ❑ Four sets of four 2-bit NOR predecoders = $4 \times 4 \times (2+2) = 64$
 - ❑ 256 word line drivers, each a four input NAND – $256 \times (4+4) = 2,048$
 - 4,096 vs 2,112 = almost a 50% savings
- ❑ Number of inputs to the gates driving the WLs is halved, so the propagation delay is reduced by a factor of ~4

Split Row Two-Level 8x256 Decoder
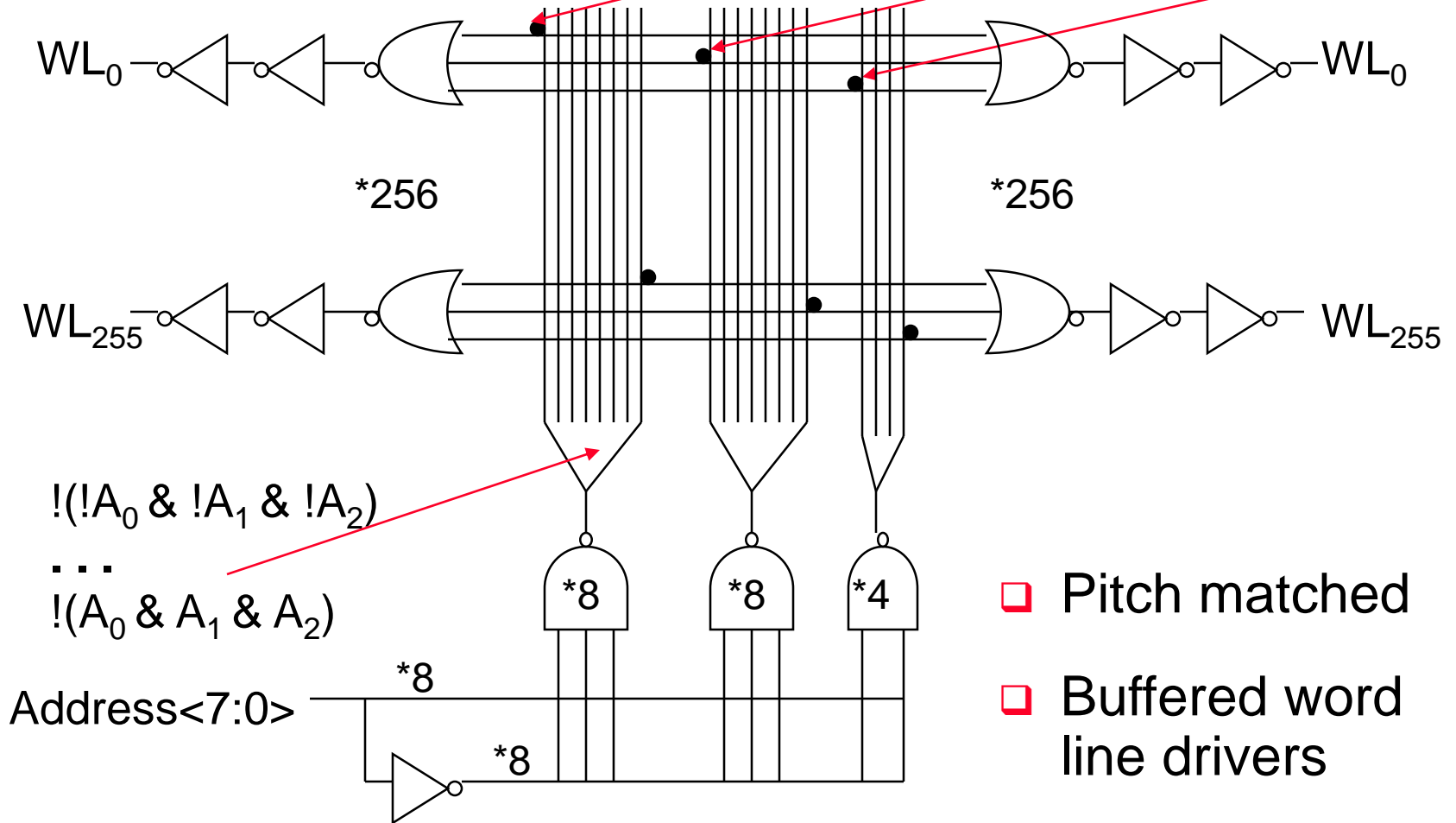
$$\overline{(\overline{(\overline{A_0} \& \overline{A_1} \& \overline{A_2})} \mid \overline{(\overline{A_3} \& \overline{A_4} \& \overline{A_5})} \mid \overline{(\overline{A_6} \& \overline{A_7})})}$$




Pass Transistor Based Column Decoder

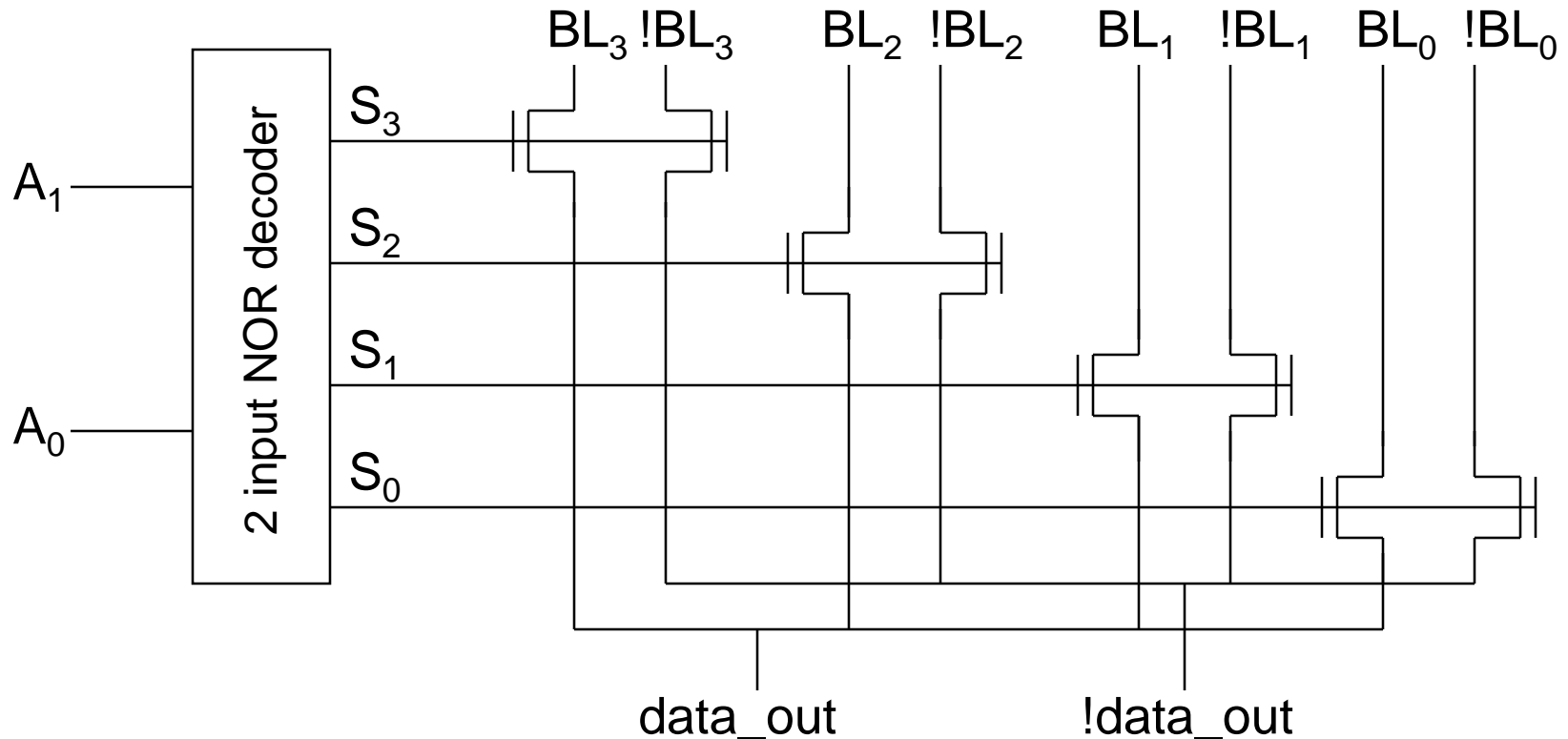

- Read: connect BLs to the Sense Amps (SA) Writes:
drive one of the BLs low to write a 0 into the cell
- Fast since there is only one transistor in the signal path. However, there is a large transistor count ($(K+1)2^K + 2 \times 2^K$)
- For $K = 2 \rightarrow 3 \times 2^2$ (decoder) + 2×2^2 (PTs) = $12 + 8 = 20$

Tree Based Column Decoder

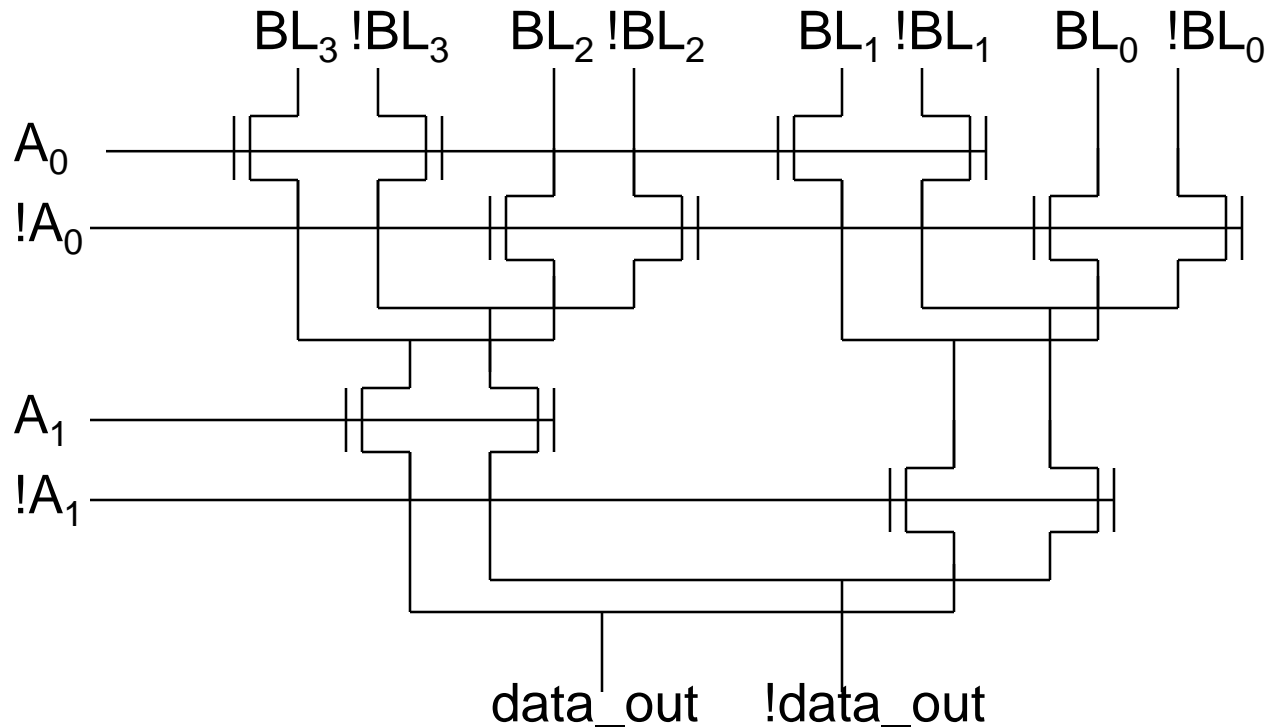

- ❑ Number of transistors reduced to $(2 \times 2 \times (2^K - 1))$
 - for $K = 2 \rightarrow 2 \times 2 \times (2^2 - 1) = 4 \times 3 = 12$
- ❑ Delay increases quadratically with the number of sections (K) (so prohibitive for large decoders)
 - can fix with buffers, progressive sizing, combination of tree and pass transistor approaches


Decoder Complexity Comparisons

- Consider a memory with 10b address and 8b data

Conf.	Data/Row	Row Decoder	Column Decoder
1D	8b	10b = a 10×2^{10} decoder Single stage = 20,480 Two stage = 10,320	
2D	32b (32x256 core)	8b = 8×2^8 decoder Single stage = 4,096 T Two stage = 2,112 T	2b = 2×2^2 decoder PT = 76 T Tree = 96 T
2D	64b (64x128 core)	7b = 7×2^7 decoder Single stage = 1,792 T Two stage = 1,072 T	3b = 3×2^3 decoder PT = 160 T Tree = 224 T
2D	128b (128x64 core)	6b = 6×2^6 decoder Single stage = 768 T Two stage = 432 T	4b = 4×2^4 decoder PT = 336 T Tree = 480 T

Bit Line Precharge Logic

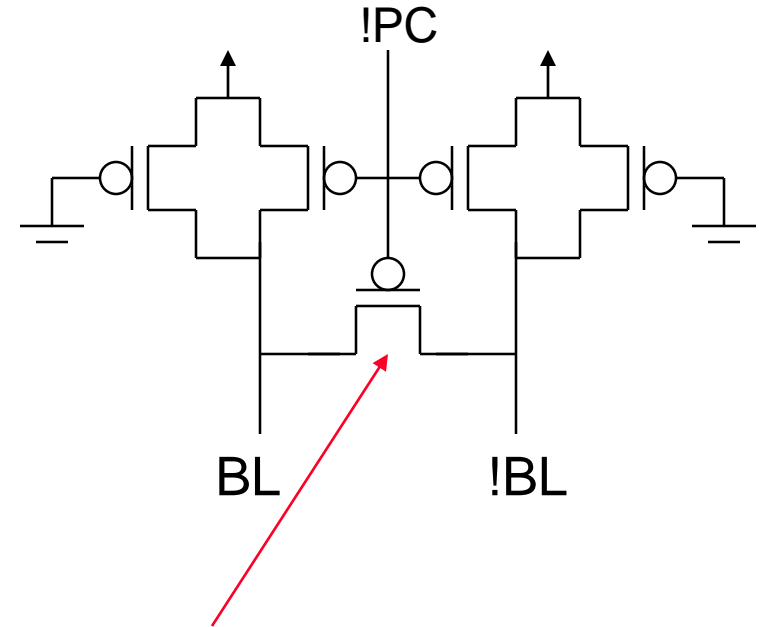
- First step of a Read cycle is to precharge (PC) the bit lines to V_{DD}
 - every differential signal in the memory must be equalized to the same voltage level before Read
- Turn off PC and enable the WL
 - the grounded PMOS load limits the bit line swing (speeding up the next precharge cycle)



equalization transistor - speeds up equalization of the two bit lines by allowing the capacitance and pull-up device of the nondischarged bit line to assist in precharging the discharged line

Sense Amplifiers

 - Amplification – resolves data with small bit line swings (in some DRAMs required for proper functionality)



- Delay reduction – compensates for the limited drive capability of the memory cell to accelerate BL transition

$$t_p = (C * \Delta V) / I_{av}$$

Annotations for the equation:


- Red arrow pointing to C : large
- Red arrow pointing to ΔV : make ΔV as small as possible
- Red arrow pointing to I_{av} : small

- Power reduction – eliminates a large part of the power dissipation due to charging and discharging bit lines
- Signal restoration – for DRAMs, need to drive the bit lines full swing after sensing (read) to do data refresh


Classes of Sense Amplifiers

- ❑ Differential SA – takes small signal differential inputs (BL and !BL) and amplifies them to a large signal single-ended output
 - ❑ common-mode rejection – rejects noise that is equally injected to both inputs
- ❑ Only suitable for SRAMs (with BL and !BL)
- ❑ Types
 - ❑ Current mirroring
 - ❑ Two-stage
 - ❑ Latch based
- ❑ Single-ended SA – needed for DRAMs


Latch Based Sense Amplifier

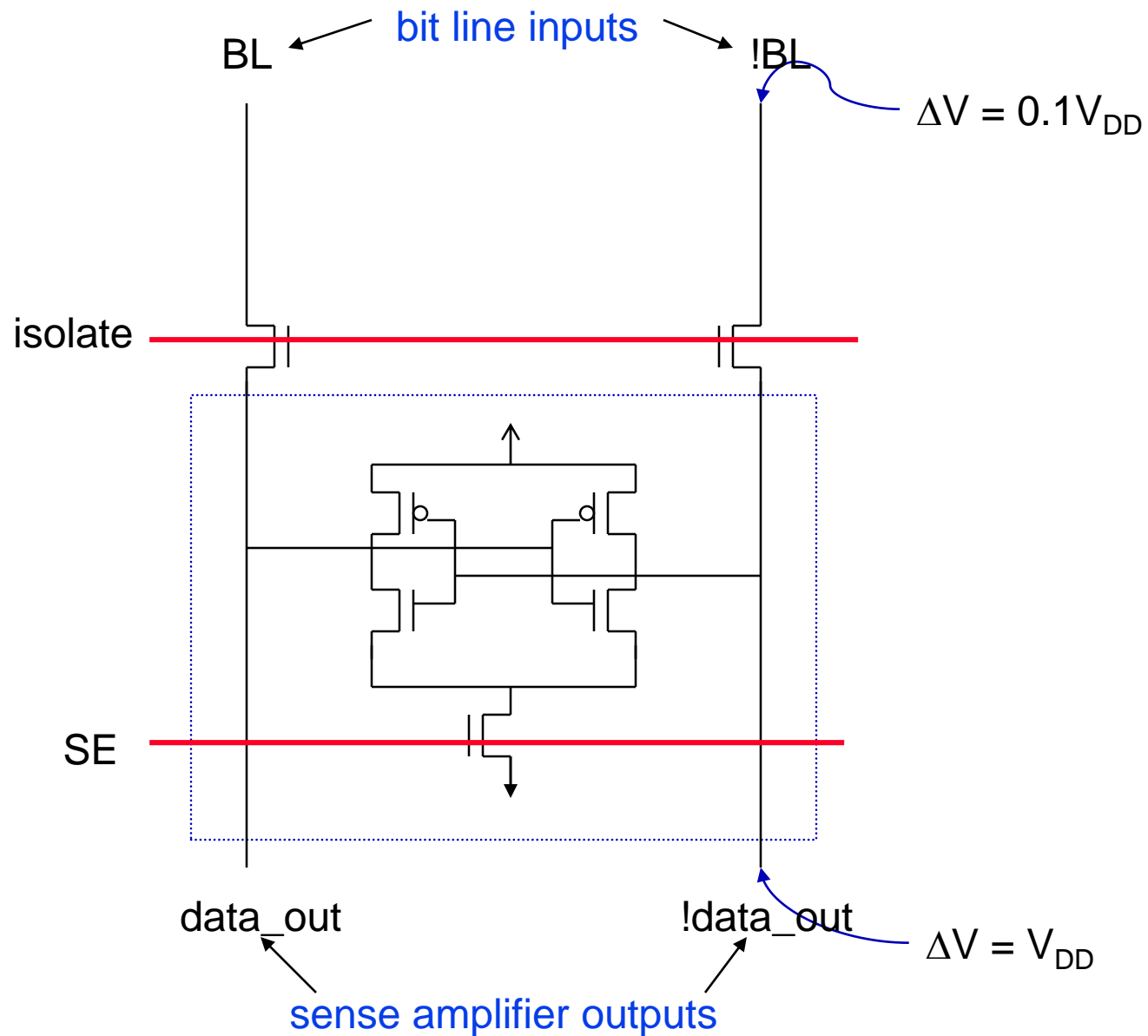

Alpha Differential Amplifier/Latch

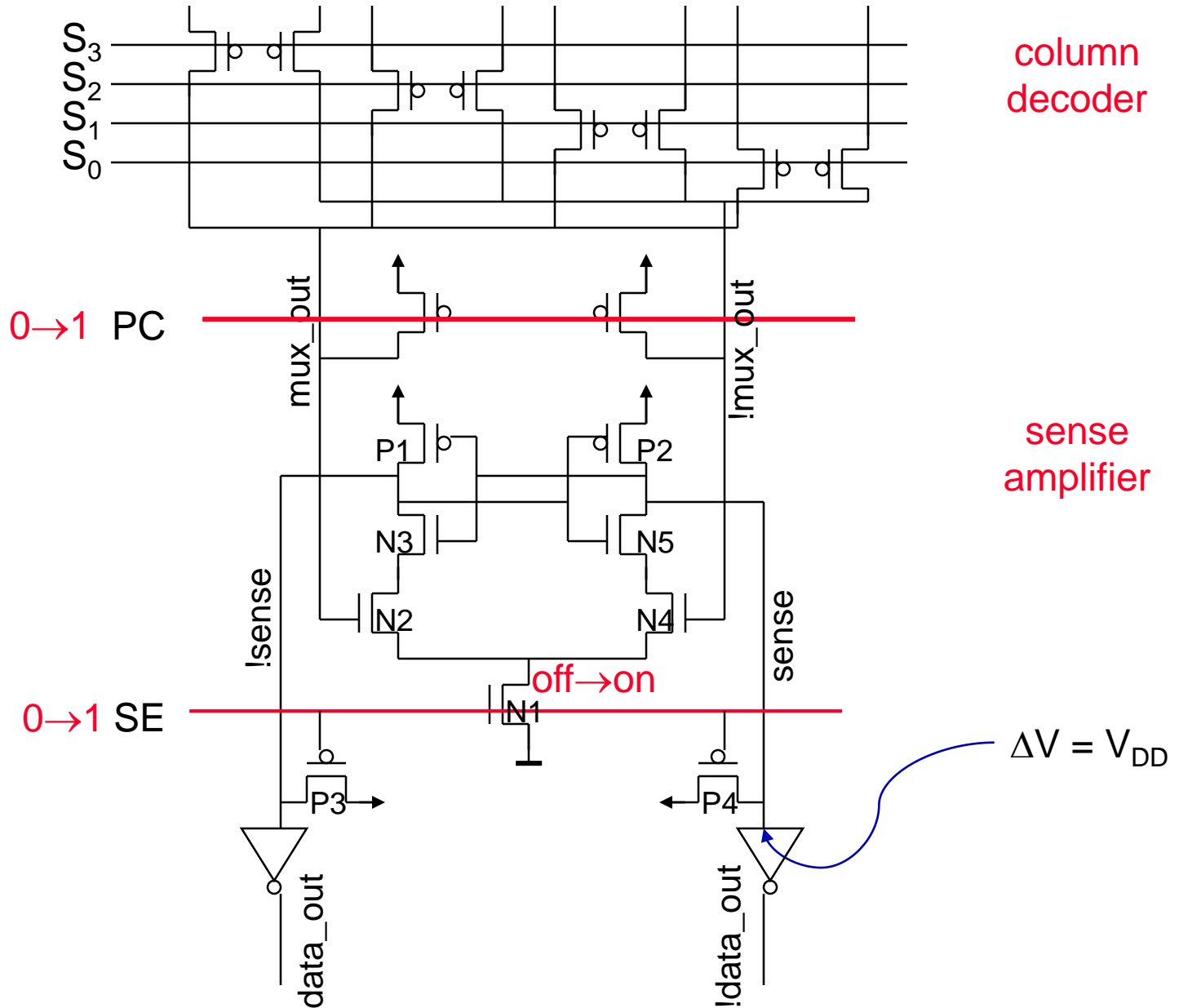

Read/Write Circuitry

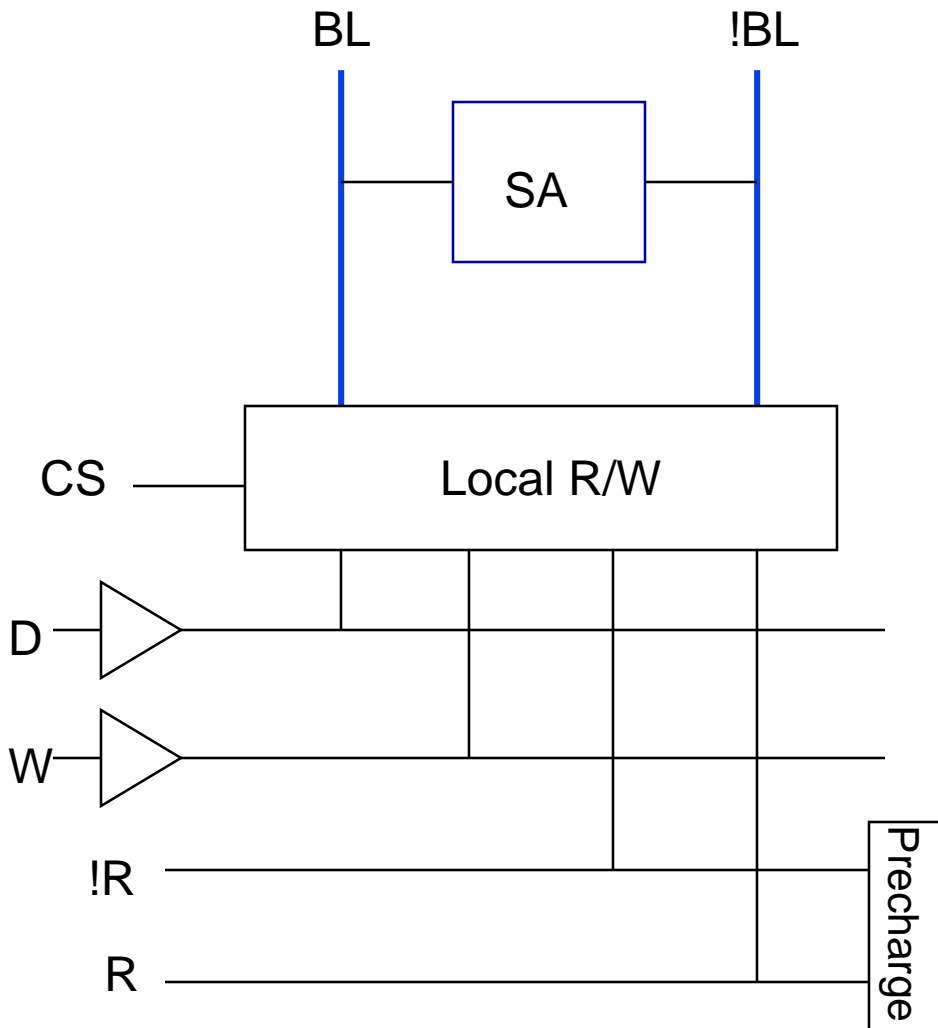


D: data (write) bus
R: read bus
W: write signal
CS: column select
(column decoder)

Local W (write):
 $BL = D, !BL = !D$
enabled by W & CS

Local R (read):
 $R = BL, !R = !BL$
enabled by !W & CS

Approaches to Memory Timing

SRAM Timing Self-Timed

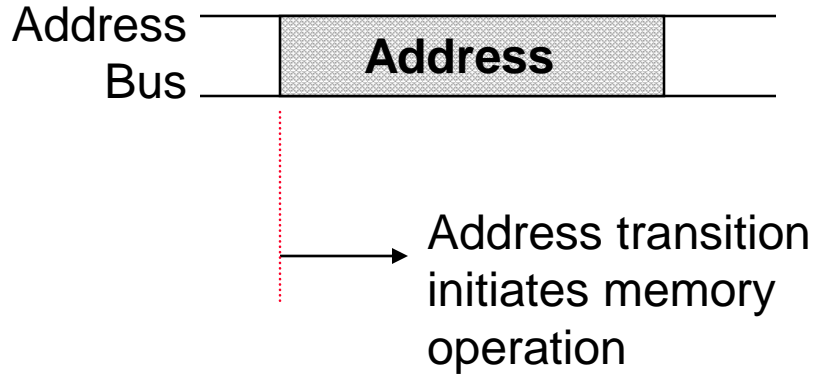

DRAM Timing Multiplexed Addressing

