

Lecture 7: Power

Outline

- ❑ Power and Energy
- ❑ Dynamic Power
- ❑ Static Power

Power and Energy

- ❑ Power is drawn from a voltage source attached to the V_{DD} pin(s) of a chip.
- ❑ Instantaneous Power: $P(t) =$
- ❑ Energy: $E =$
- ❑ Average Power: $P_{avg} =$

Power in Circuit Elements

$$P_{VDD}(t) = I_{DD}(t)V_{DD}$$



$$P_R(t) = \frac{V_R^2(t)}{R} = I_R^2(t)R$$



$$\begin{aligned} E_C &= \int_0^{\infty} I(t)V(t)dt = \int_0^{\infty} C \frac{dV}{dt} V(t)dt \\ &= C \int_0^{V_C} V(t)dV = \frac{1}{2} CV_C^2 \end{aligned}$$



Charging a Capacitor

- When the gate output rises
 - Energy stored in capacitor is
 - But energy drawn from the supply is


$$E_C = \frac{1}{2} C_L V_{DD}^2$$

$$E_{VDD} = \int_0^{\infty} I(t) V_{DD} dt = \int_0^{\infty} C_L \frac{dV}{dt} V_{DD} dt$$

$$= C_L V_{DD} \int_0^{V_{DD}} dV = C_L V_{DD}^2$$


- Half the energy from V_{DD} is dissipated in the pMOS transistor as heat, other half stored in capacitor

 - When the gate output falls
 - Energy in capacitor is dumped to GND
 - Dissipated as heat in the nMOS transistor



Switching Waveforms

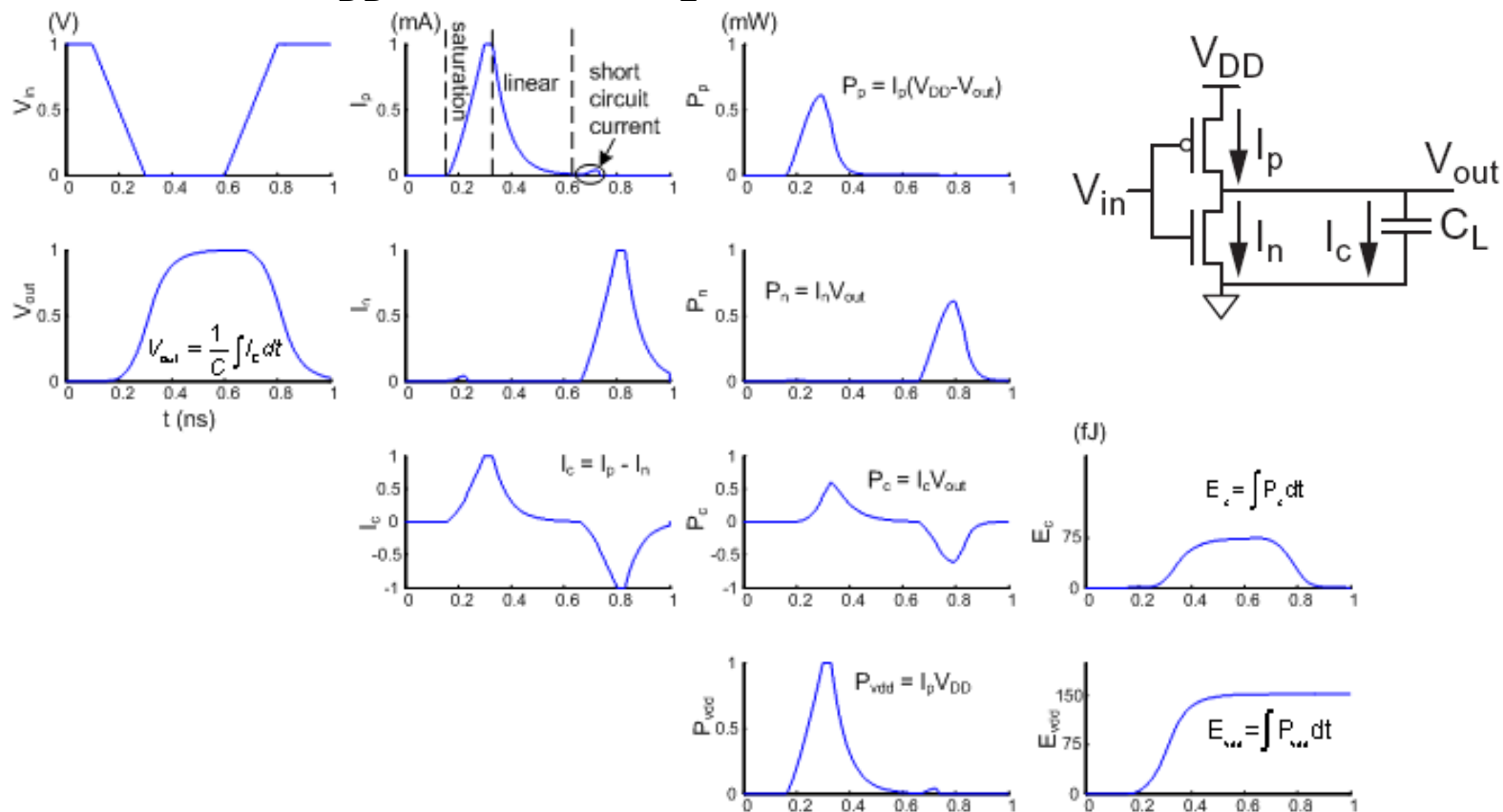□ Example: $V_{DD} = 1.0 \text{ V}$, $C_L = 150 \text{ fF}$, $f = 1 \text{ GHz}$




Switching Power

$$P_{\text{switching}} = \frac{1}{T} \int_0^T i_{DD}(t) V_{DD} dt$$

$$= \frac{V_{DD}}{T} \int_0^T i_{DD}(t) dt$$

$$= \frac{V_{DD}}{T} [T f_{\text{sw}} C V_{DD}]$$

$$= C V_{DD}^2 f_{\text{sw}}$$

 

Activity Factor

- ❑ Suppose the system clock frequency = f
- ❑ Let $f_{sw} = \alpha f$, where α = activity factor
 - If the signal is a clock, $\alpha = 1$
 - If the signal switches once per cycle, $\alpha = 1/2$
- ❑ Dynamic power:
$$P_{\text{switching}} = \alpha C V_{DD}^2 f$$

Short Circuit Current

- ❑ When transistors switch, both nMOS and pMOS networks may be momentarily ON at once
- ❑ Leads to a blip of “short circuit” current.
- ❑ $< 10\%$ of dynamic power if rise/fall times are comparable for input and output
- ❑ We will generally ignore this component

Power Dissipation Sources

- ❑ $P_{\text{total}} = P_{\text{dynamic}} + P_{\text{static}}$
- ❑ Dynamic power: $P_{\text{dynamic}} = P_{\text{switching}} + P_{\text{shortcircuit}}$
 - Switching load capacitances
 - Short-circuit current
- ❑ Static power: $P_{\text{static}} = (I_{\text{sub}} + I_{\text{gate}} + I_{\text{junct}} + I_{\text{contention}})V_{\text{DD}}$
 - Subthreshold leakage
 - Gate leakage
 - Junction leakage
 - Contention current

Dynamic Power Example

- ❑ 1 billion transistor chip
 - 50M logic transistors
 - Average width: 12λ
 - Activity factor = 0.1
 - 950M memory transistors
 - Average width: 4λ
 - Activity factor = 0.02
 - 1.0 V 65 nm process
 - $C = 1 \text{ fF}/\mu\text{m}$ (gate) + $0.8 \text{ fF}/\mu\text{m}$ (diffusion)
- ❑ Estimate dynamic power consumption @ 1 GHz.
Neglect wire capacitance and short-circuit current.

Solution

$$C_{\text{logic}} = (50 \times 10^6)(12\lambda)(0.025\mu\text{m} / \lambda)(1.8 \text{ fF} / \mu\text{m}) = 27 \text{ nF}$$

$$C_{\text{mem}} = (950 \times 10^6)(4\lambda)(0.025\mu\text{m} / \lambda)(1.8 \text{ fF} / \mu\text{m}) = 171 \text{ nF}$$

$$P_{\text{dynamic}} = \left[0.1C_{\text{logic}} + 0.02C_{\text{mem}} \right] (1.0)^2 (1.0 \text{ GHz}) = 6.1 \text{ W}$$

Dynamic Power Reduction

□ $P_{\text{switching}} = \alpha C V_{DD}^2 f$

□ Try to minimize:

- Activity factor
- Capacitance
- Supply voltage
- Frequency

Activity Factor Estimation

Activity factor of a node is the probability that it switches from 0 to 1.

□ Define P_i to be the probability that node i is 1.

– $P_i = 1 - P_i$ is the probability that node i is 0.

□ $\alpha_i = P_i * P_i$; the activity factor of node i , is the probability that the node is 0 on one cycle and 1 on the next

□ Completely random data has $P = 0.5$ and $\alpha = 0.25$

□ Data propagating through ANDs and ORs has lower activity factor

– Depends on design, but typically $\alpha \approx 0.1$


Switching Probability

Gate	P_Y
AND2	$P_A P_B$
AND3	$P_A P_B P_C$
OR2	$1 - \bar{P}_A \bar{P}_B$
NAND2	$1 - P_A P_B$
NOR2	$\bar{P}_A \bar{P}_B$
XOR2	$P_A \bar{P}_B + \bar{P}_A P_B$

 Example

Determine the Activity Factors at each node:


- ❑ A 4-input AND is built out of two levels of gates
- ❑ Estimate the activity factor at each node if the inputs have $P = 0.5$



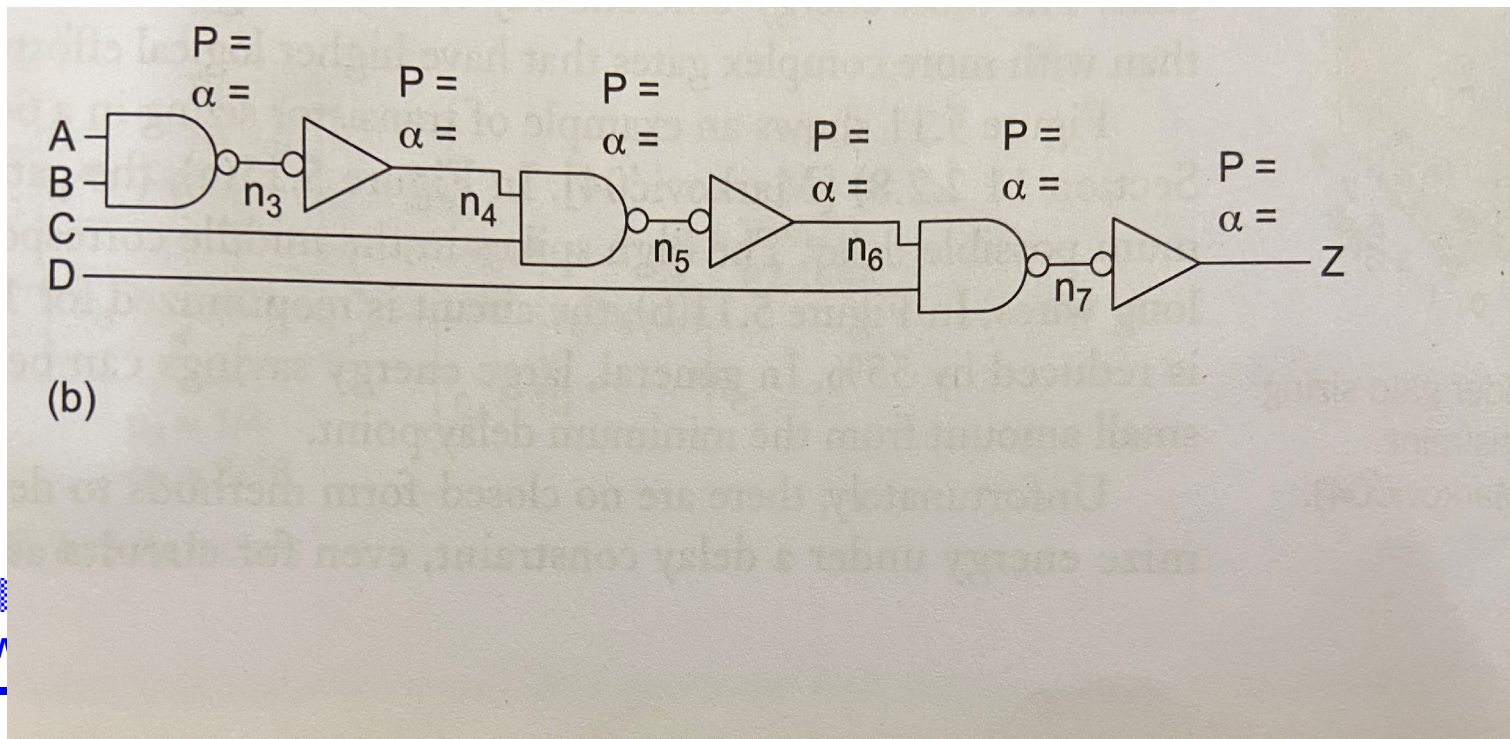Example

Determine the Activity Factors at each node:


- ❑ A chain of gates
- ❑ Estimate the activity factor at each node if the inputs have $P = 0.5$



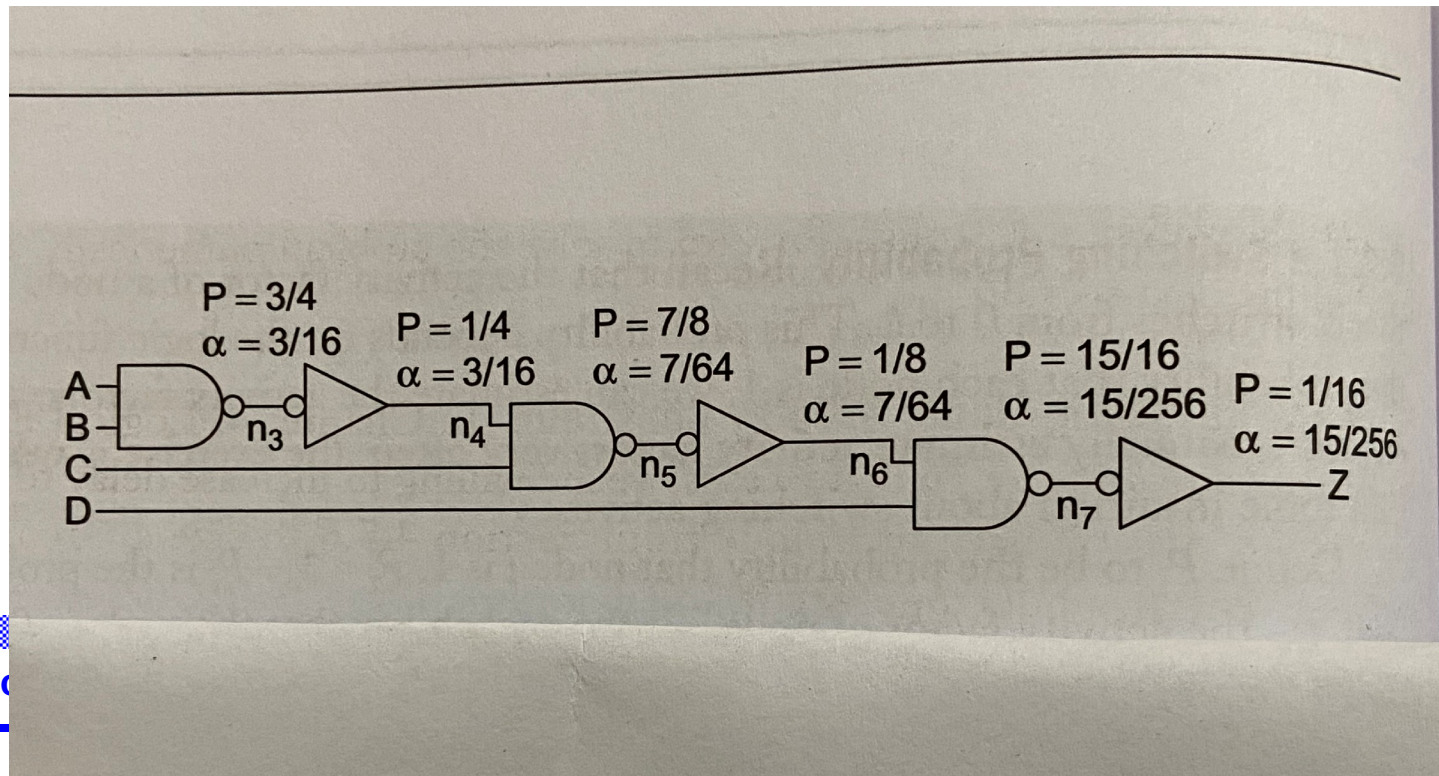Example


Determine the Activity Factors at each node:

- ❑ A chain of gates
- ❑ Estimate the activity factor at each node if the inputs have $P = 0.5$



Clock Gating

 - ❑ The best way to reduce the activity is to turn off the clock to registers in unused blocks
 - Saves clock activity ($\alpha = 1$)
 - Eliminates all switching activity in the block
 - Requires determining if block will be used



Capacitance

- ❑ Gate capacitance

Device-Switching capacitance is reduced by

- Fewer stages of logic
- Small gate sizes

- ❑ Wire capacitance

- Good floorplanning to keep communicating blocks close to each other
- Drive long wires with inverters or buffers rather than complex gates

Gate Sizing under a Delay Constraint

Consider a model to compute the energy of a circuit. If a unit inverter has gate capacitance $3C$, then a gate with logical effort g , parasitic delay p , and drive x has gx times as much gate capacitance and px times as much diffusion capacitance. The energy of the entire circuit:



$$\text{Energy} = 3CV_{DD}^2 \sum_{i \in \text{nodes}} \alpha_i (C_{\text{wire}}/3c + p_i x_i + \sum_{j \in \text{fanout}(i)} g_j x_j)$$

$$= \sum_{i \in \text{nodes}} \alpha_i (c_i + p_i x_i + \sum_{j \in \text{fanout}(i)} g_j x_j)$$

$$= \sum_{i \in \text{nodes}} \alpha_i x_i d_i)$$

Voltage / Frequency

  - ❑ Run each block at the lowest possible voltage and frequency that meets performance requirements
- ❑ Voltage Domains
 - Provide separate supplies to different blocks
 - Level converters required when crossing from low to high V_{DD} domains
- ❑ Dynamic Voltage Scaling
 - Adjust V_{DD} and f according to workload



Static Power

- ❑ Static power is consumed even when chip is not switching.
 - Leakage draws power from nominally OFF devices
 - Leakage power was of concern primarily during sleep mode and it was negligible compared to dynamic power.
 - In nanometer processes with low threshold voltages and thin gate oxides, leakage can account for as much as a third of total active power.

Static Power Sources

- ❑ Static power arises from
 - Subthreshold leakage
 - Gate leakage
 - Junction leakage
 - Contention current


Static power: $P_{\text{static}} = (I_{\text{sub}} + I_{\text{gate}} + I_{\text{junct}} + I_{\text{contention}})V_{\text{DD}}$

Leakage Sources

- ❑ Subthreshold conduction
 - Transistors can't abruptly turn ON or OFF
 - Dominant source in contemporary transistors
- ❑ Gate leakage
 - Tunneling through ultrathin gate dielectric
- ❑ Junction leakage
 - Reverse-biased PN junction diode current

Leakage

 - ❑ What about current in cutoff?
 - Current doesn't go to 0 in cutoff




Subthreshold Leakage

- Subthreshold leakage exponential with V_{gs}

$$I_{ds} = I_{ds0} e^{\frac{V_{gs} - V_{t0} + \eta V_{ds} - k_y V_{sb}}{n v_T}} \left(1 - e^{-\frac{V_{ds}}{v_T}} \right)$$

- n is process dependent
 - typically 1.3-1.7
- Rewrite relative to I_{off} on log scale

 
$$I_{ds} = I_{off} 10^{\frac{V_{gs} + \eta(V_{ds} - V_{dd}) - k_y V_{sb}}{S}} \left(1 - e^{-\frac{V_{ds}}{v_t}} \right) \quad S = \left[\frac{d(\log_{10} I_{ds})}{dV_{gs}} \right]^{-1} = n v_T \ln 10$$



- $S \approx 100$ mV/decade @ room temperature
- DIBL – Drain Induced Barrier Lowering, GIDL – Gate-Induced Drain Leakage


Drain Induced Barrier Lowering

 - ❑ V_{ds} creates an electric field that affects the threshold voltage $V_t = V_{t0} - \eta V_{ds}$, η is DIBL coefficient, typical value is 0.1.
- ❑ DIBL causes I_{ds} to increase with V_{ds} in saturation.



Gate-Induced Drain Leakage

 - ❑ Occurs at overlap between gate and drain
 - Most pronounced when drain is at V_{DD} , gate is at a negative voltage
 - Thwarts efforts to reduce subthreshold leakage using a negative gate voltage



Subthreshold Leakage

- For $V_{ds} > 50 \text{ mV}$

$$I_{sub} \approx I_{off} 10^{\frac{V_{gs} + \eta(V_{ds} - V_{DD}) - k_y V_{sb}}{S}}$$

- I_{off} = leakage at $V_{gs} = 0$, $V_{ds} = V_{DD}$

Typical values in 65 nm

$$I_{off} = 100 \text{ nA}/\mu\text{m} @ V_t = 0.3 \text{ V}$$

$$I_{off} = 10 \text{ nA}/\mu\text{m} @ V_t = 0.4 \text{ V}$$

$$I_{off} = 1 \text{ nA}/\mu\text{m} @ V_t = 0.5 \text{ V}$$

$$\eta = 0.1$$

$$k_y = 0.1$$

$$S = 100 \text{ mV/decade}$$

Leakage Control

- ❑ Leakage and delay trade off
 - Aim for low leakage in sleep and low delay in active mode
- ❑ To reduce leakage:
 - Increase V_t : *multiple* V_t
 - Use low V_t only in critical circuits
 - Increase V_s : *stack effect*
 - *Input vector control* in sleep
 - Decrease V_b
 - *Reverse body bias* in sleep
 - Or forward body bias in active mode

Stack Effect


- Series OFF transistors have less leakage

- $V_x > 0$, so N2 has negative V_{gs}

$$I_{sub} = I_{off} N1 \cdot 10^{\frac{\eta(V_x - V_{DD})}{S}} = I_{off} N2 \cdot 10^{\frac{-V_x + \eta((V_{DD} - V_x) - V_{DD}) - k_y V_x}{S}}$$

$$V_x = \frac{\eta V_{DD}}{1 + 2\eta + k_y}$$

 
$$I_{sub} = I_{off} \cdot 10^{\frac{-\eta V_{DD} \left(\frac{1+\eta+k_y}{1+2\eta+k_y} \right)}{S}} \approx I_{off} \cdot 10^{\frac{-\eta V_{DD}}{S}}$$



- Leakage through 2-stack reduces ~10x
- Leakage through 3-stack reduces further

Junction Leakage

 - ❑ Reverse-biased p-n junctions have some leakage
 - Ordinary diode leakage
 - Band-to-band tunneling (BTBT)
 - Gate-induced drain leakage (GIDL)



Diode Leakage

- ❑ Reverse-biased p-n junctions have some leakage

$$I_D = I_S \left(e^{\frac{V_D}{V_T}} - 1 \right)$$

- ❑ At any significant negative diode voltage, $I_D = -I_S$
- ❑ I_S depends on doping levels
 - And area and perimeter of diffusion regions
 - Typically $< 1 \text{ fA}/\mu\text{m}^2$ (negligible)

Band-to-Band Tunneling

- ❑ Tunneling across heavily doped p-n junctions
 - Especially sidewall between drain & channel when *halo doping* is used to increase V_t
- ❑ Increases junction leakage to significant levels

$$I_{BTBT} = WX_j A \frac{E_j}{E_g^{0.5}} V_{dd} e^{-B \frac{E_g^{1.5}}{E_j}}$$

$$E_j = \sqrt{\frac{2qN_{halo}N_{sd}}{\epsilon(N_{halo} + N_{sd})}} \left(V_{DD} + v_T \ln \frac{N_{halo}N_{sd}}{n_i^2} \right)$$

- X_j : sidewall junction depth
- E_g : bandgap voltage
- A, B : tech constants

Junction Leakage

- ❑ From reverse-biased p-n junctions
 - Between diffusion and substrate or well
- ❑ Ordinary diode leakage is negligible
- ❑ Band-to-band tunneling (BTBT) can be significant
 - Especially in high- V_t transistors where other leakage is small
 - Worst at $V_{db} = V_{DD}$
- ❑ Gate-induced drain leakage (GIDL) exacerbates
 - Worst for $V_{gd} = -V_{DD}$ (or more negative)


Gate Leakage

- ❑ Carriers tunnel thorough very thin gate oxides
- ❑ Exponentially sensitive to t_{ox} and V_{DD}

$$I_{gate} = WA \left(\frac{V_{DD}}{t_{ox}} \right)^2 e^{-B \frac{t_{ox}}{V_{DD}}}$$

- A and B are tech constants
- Greater for electrons
 - So nMOS gates leak more

 - ❑ Negligible for older processes ($t_{ox} > 20 \text{ \AA}$)
- ❑ Critically important at 65 nm and below ($t_{ox} \approx 10.5 \text{ \AA}$)



From [Song01]

Gate Leakage


- ❑ Extremely strong function of t_{ox} and V_{gs}
 - Negligible for older processes
 - Approaches subthreshold leakage at 65 nm and below in some processes
- ❑ An order of magnitude less for pMOS than nMOS
- ❑ Control leakage in the process using $t_{ox} > 10.5 \text{ \AA}$
 - High-k gate dielectrics help
 - Some processes provide multiple t_{ox}
 - e.g. thicker oxide for 3.3 V I/O transistors
- ❑ Control leakage in circuits by limiting V_{DD}

NAND3 Leakage Example

□ 100 nm process

$$I_{gn} = 6.3 \text{ nA} \quad I_{gp} = 0$$
 
$$I_{offn} = 5.63 \text{ nA} \quad I_{offp} = 9.3 \text{ nA}$$



Input State (ABC)	I_{sub}	I_{gate}	I_{total}	V_x	V_z
000	0.4	0	0.4	stack effect	stack effect
001	0.7	0	0.7	stack effect	$V_{DD} - V_t$
010	0.7	1.3	2.0	intermediate	intermediate
011	3.8	0	3.8	$V_{DD} - V_t$	$V_{DD} - V_t$
100	0.7	6.3	7.0	0	stack effect
101	3.8	6.3	10.1	0	$V_{DD} - V_t$
110	5.6	12.6	18.2	0	0
111	28	18.9	46.9	0	0

Data from [Lee03]

Contention Current

- ❑ Static CMOS Circuits have no contention current
- ❑ However, pseudo nMOS gates experience contention between the nMOS pulldown and the always-on pMOS pull-ups, when the output is 0.
- ❑ Current mode logic and many analog circuits also draw static current
- ❑ Such circuits should be turned off in sleep mode by disabling the pull-ups or current source.

Static Power Estimation

- ❑ Static power estimation is done by estimating the total width of transistors that are leaking , multiplying by the leakage current per width and multiplying by the fraction of transistors that are in their leaky state (usually one-half)
- ❑ Add the contention current if applicable
- ❑ The static power is the supply voltage times the static current

Static Power Example

- ❑ Revisit power estimation for 1 billion transistor chip
- ❑ Estimate static power consumption
 - Subthreshold leakage
 - Normal V_t : 100 nA/ μm
 - High V_t : 10 nA/ μm
 - High V_t used in all memories and in 95% of logic gates
 - Gate leakage 5 nA/ μm
 - Junction leakage negligible

Solution

$$W_{\text{normal-}V_t} = (50 \times 10^6)(12\lambda)(0.025\mu\text{m} / \lambda)(0.05) = 0.75 \times 10^6 \mu\text{m}$$

$$W_{\text{high-}V_t} = \left[(50 \times 10^6)(12\lambda)(0.95) + (950 \times 10^6)(4\lambda) \right] (0.025\mu\text{m} / \lambda) = 109.25 \times 10^6 \mu\text{m}$$

$$I_{\text{sub}} = \left[W_{\text{normal-}V_t} \times 100 \text{ nA}/\mu\text{m} + W_{\text{high-}V_t} \times 10 \text{ nA}/\mu\text{m} \right] / 2 = 584 \text{ mA}$$


$$I_{\text{gate}} = \left[(W_{\text{normal-}V_t} + W_{\text{high-}V_t}) \times 5 \text{ nA}/\mu\text{m} \right] / 2 = 275 \text{ mA}$$

$$P_{\text{static}} = (584 \text{ mA} + 275 \text{ mA})(1.0 \text{ V}) = 859 \text{ mW}$$

Power Gating

- ❑ Turn OFF power to blocks when they are idle to save leakage

 - Use virtual V_{DD} (V_{DDV})
- Gate outputs to prevent invalid logic levels to next block



- ❑ Voltage drop across sleep transistor degrades performance during normal operation
 - Size the transistor wide enough to minimize impact
- ❑ Switching wide sleep transistor costs dynamic power
 - Only justified when circuit sleeps long enough